

$T_1, T_3, T_5 \rightarrow$  Positive group.

$T_4, T_6, T_2 \rightarrow$  Negative group.

i) For  $\alpha = 0^\circ$ .

$$T_1 \rightarrow 30^\circ$$

$$T_2 \rightarrow 90^\circ$$

$$T_3 \rightarrow 150^\circ$$

$$T_4 \rightarrow 210^\circ$$

$$T_5 \rightarrow 270^\circ$$

$$T_6 \rightarrow 330^\circ$$

$$\alpha = 0^\circ$$

$$\alpha = 30^\circ$$

$$\alpha = 60^\circ$$

$$\alpha = 90^\circ$$

$$\frac{\pi}{6}$$

$$\frac{\pi}{6} + 30^\circ$$

$$\frac{\pi}{6} + 60^\circ$$

$$\frac{\pi}{6} + 90^\circ$$

$v_{ab}$   
+

$$\frac{\pi}{2}$$

$$\frac{\pi}{2} + 30^\circ$$

$$\frac{\pi}{2} + 60^\circ$$

$$\frac{\pi}{2} + 90^\circ$$

Average output voltage,

$$V_o(\text{avg}) = \frac{1}{T} \int_0^T V_o(t) dt.$$

Conclusions:-

1. For  $0 < \alpha < 90^\circ$ , the output voltage is positive.
2. For  $\alpha = 90^\circ$ , the average output voltage is zero.
3. For  $90^\circ < \alpha < 180^\circ$ , the output voltage is negative.

Expression for output voltage:

$$V_a = V_m \sin \omega t$$

$$V_b = V_m \sin(\omega t - 120^\circ)$$

$$V_c = V_m \sin(\omega t - 240^\circ).$$

where,  $V_m$  - max/peak phase voltage

Then,  $V_{ab} = V_m \sin(\omega t + 30^\circ)$

$$V_{bc} = V_m \sin(\omega t - 90^\circ)$$

$$V_{ca} = V_m \sin(\omega t - 210^\circ)$$

$$\begin{aligned}
V_{o(\text{avg})} &= \frac{1}{(\pi/3)} \int_{\alpha+\pi/6}^{\alpha+\pi/2} V_{ab} dt. \\
&= \frac{3}{\pi} \int_{\alpha+\pi/6}^{\alpha+\pi/2} V_{m2} \sin(\omega t + 30^\circ) d(\omega t) \\
&= \frac{3V_{m2}}{\pi} \left[ -\cos(\omega t + 30^\circ) \right]_{\alpha+\pi/6}^{\alpha+\pi/2} \\
&= \frac{3V_{m2}}{\pi} \left[ -\cos\left[\frac{\pi}{2} + \alpha + \frac{\pi}{6}\right] + \cos\left[\frac{\pi}{6} + \alpha + \frac{\pi}{6}\right] \right] \\
&= \frac{3V_{m2}}{\pi} \left[ -\cos\left(\alpha + \frac{2\pi}{3}\right) + \cos\left(\alpha + \frac{\pi}{3}\right) \right] \\
&= \frac{3V_{m2}}{\pi} \left[ -\cos\left[\alpha + \left(\pi - \frac{\pi}{3}\right)\right] + \cos\left(\alpha + \frac{\pi}{3}\right) \right] \\
&= \frac{3V_{m2}}{\pi} \left[ \cos\left(\alpha - \frac{\pi}{3}\right) + \cos\left(\alpha + \frac{\pi}{3}\right) \right] \\
&= \frac{3V_{m2}}{\pi} \left[ 2\cos\alpha \cdot \cos\frac{\pi}{3} \right]
\end{aligned}$$

$$\therefore V_{o(\text{avg})} = \frac{3V_{m2}}{\pi} \cos\alpha$$

Since,  $V_{m2} = \sqrt{3} V_m$ .

Then,  $V_{o(\text{avg})} = \frac{3\sqrt{3} V_m \cos\alpha}{\pi}$

In terms of rms:

$$V_{\text{rms}} \rightarrow V_m$$


$$V_{\text{rms}} = V_m / \sqrt{2} \Rightarrow \boxed{V_m = \sqrt{2} V_{\text{rms}}}$$

$$\therefore V_{o(\text{avg})} = \frac{3\sqrt{3} \sqrt{2} V_{\text{rms}} \cos\alpha}{\pi}$$

$$\therefore \boxed{V_{o(\text{avg})} = \frac{3\sqrt{6} V_{\text{rms}} \cos\alpha}{\pi}}$$


31/12/15

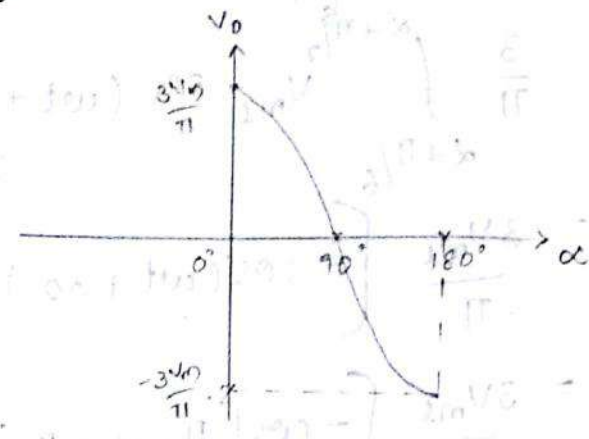For  $0 < \alpha < 90^\circ$   $V_0 = +ve$   $\alpha = 90^\circ$   $V_0 = 0$   $90^\circ < \alpha < 180^\circ$   $V_0 = -ve$





\* MODES OF OPERATION: [Thyristor never conducts in  $V_E$  in opposite direction]

MODE 1:

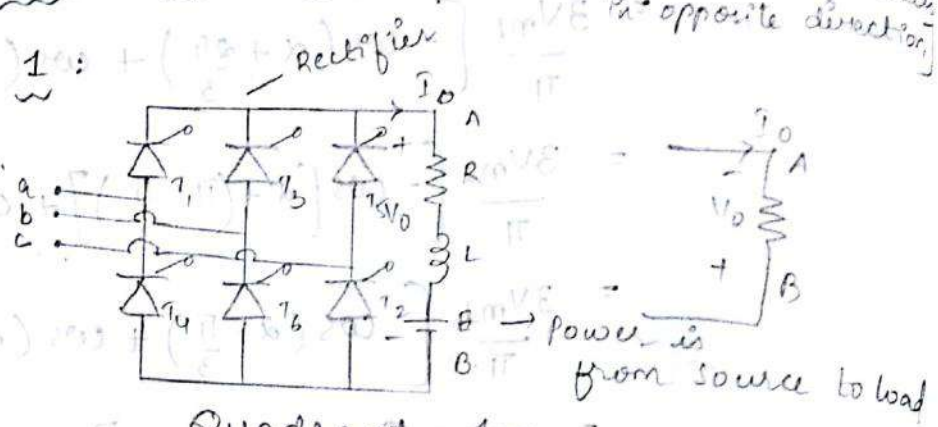


Quadrant - 1

By using single rectifier, we can get two modes of operation.

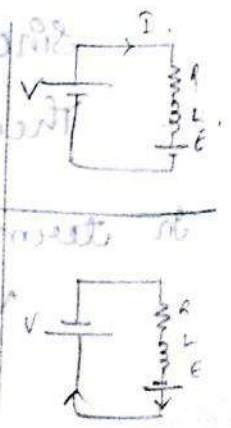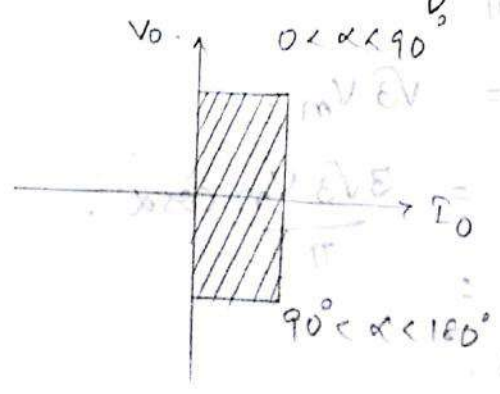



MODE 2 :

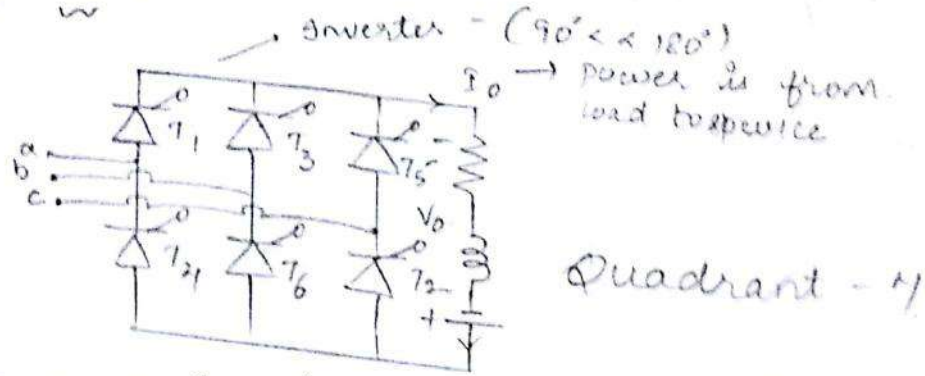

\* Torque - speed characteristics of Separately excited or Shunt motors:  
we know that,


$$\omega_m = \frac{V}{K} - \frac{(R_a) \cdot T}{K^2}$$

as we have,  $V_0 = \frac{3V_{m1} \cos \alpha}{\pi}$


Then,  $\omega_m = \frac{V_0}{K} - \frac{R_a \cdot T}{K^2}$

$$\omega_m = \frac{3V_{m1} \cos \alpha}{\pi K} - \frac{R_a \cdot T}{K^2}$$

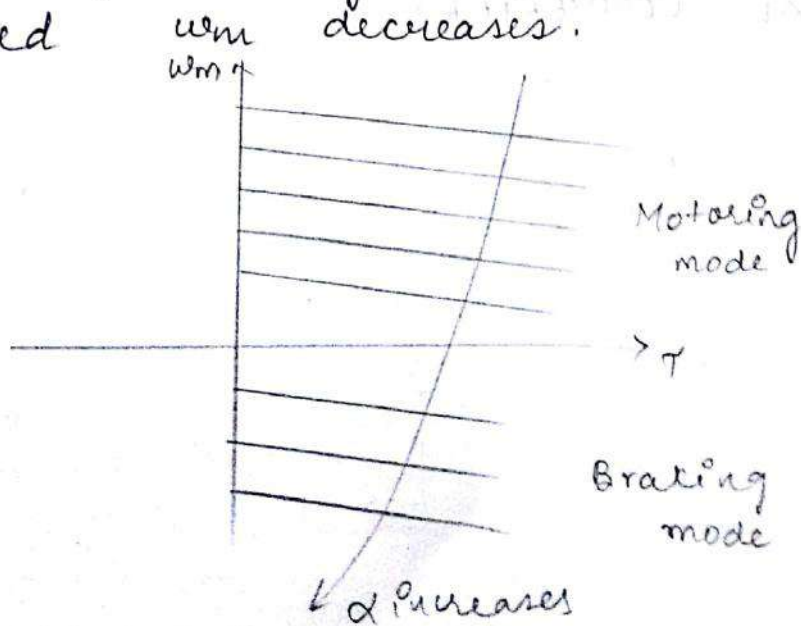as  $\alpha$  increases,  $V_0$  will get decreases  
so gradually as  $V_0 \downarrow$ , then  
speed  $\omega_m$  decreases.



# \* 3-φ CONVERTER FED SERIES MOTOR.

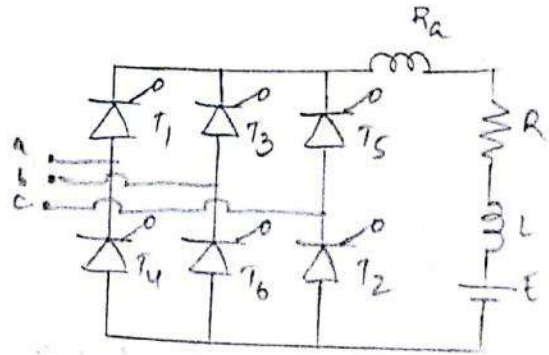


Torque - Speed characteristics:


$$\omega_m = \frac{V}{\sqrt{k_e k_f} \sqrt{T}} - \frac{R_a + R_{se}}{k_e k_f}$$

$$\omega_m = \frac{3V_{m1} \cos \alpha}{\pi} - \frac{R_a + R_{se}}{k_e k_f}$$

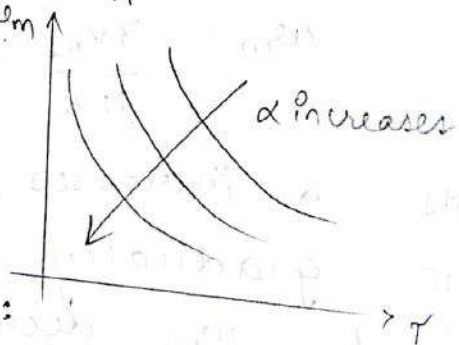As  $\alpha \uparrow$ ,  $V \downarrow$ ,  $\omega_m \downarrow$ .



# \* DUAL CONVERTER:

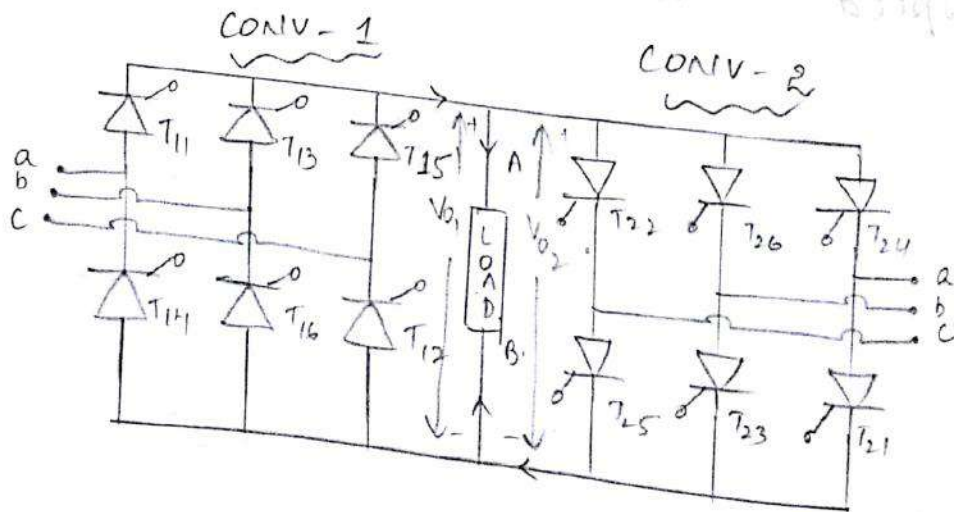

1) NON - CIRCULATING CURRENT :-

In this mode of operation, only one converter is fired / operated at a time. and the second converter will be idle.

\* FOR CONVERTER 1 :


$0 < \alpha < 90^\circ \rightarrow V_o = +ve, I_o = +ve$

$90^\circ < \alpha < 180^\circ \rightarrow V_o = -ve, I_o = +ve.$

\* FOR CONVERTER 2 :


$0 < \alpha < 90^\circ \rightarrow V_o = -ve, I_o = -ve.$

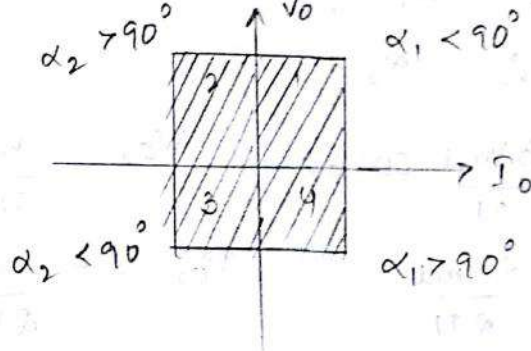$90^\circ < \alpha < 180^\circ \rightarrow V_o = +ve, I_o = -ve.$



- 1) During the changeover from 1<sup>st</sup> converter to 2<sup>nd</sup> converter ensure that load current becomes zero.
- 2) After one converter is off by taking out / blocking the firing pulses, 10 to 20 msec time should be given for the proper commutation of thyristors.

2) CIRCULATING CURRENT MODE :

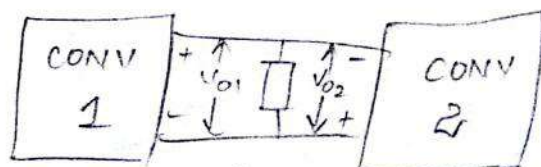

$V_{o1}$  &  $V_{o2} \rightarrow$  should be equal in magnitude & also in phase.



$$V_{o1} = -V_{o2}$$

$$\frac{3V_{m1}}{\pi} \cos \alpha_1 = -\frac{3V_{m1}}{\pi} \cos \alpha_2$$

$$\cos \alpha_1 = -\cos \alpha_2$$

$$\Rightarrow \cos \alpha_1 = \cos (180 - \alpha_2)$$

$$\therefore \alpha_1 = 180^\circ - \alpha_2$$

$$\Rightarrow \alpha_1 + \alpha_2 = 180^\circ$$

At every instant, the firing angle of two converters is equal to 180

Ex: CONV-1,  $\alpha_1 = 60^\circ$   
 CONV-2,  $\alpha_2 = 120^\circ$

$$\text{Then, } V_{o1} = \frac{3V_{m1}}{\pi} \cos 60^\circ; \quad V_{o2} = \frac{3V_{m1}}{\pi} \cos 120^\circ$$






$$\Rightarrow V_{o1} = \frac{3V_{m1}}{2\pi}; \quad V_{o2} = -\frac{3V_{m1}}{2\pi}$$

At any instant, one converter acts as a rectifier & other converter act as an inverter.



$0 < \alpha_1 < 90^\circ \rightarrow$  Rectifier  $\rightarrow 0 < \alpha_2 < 90^\circ$

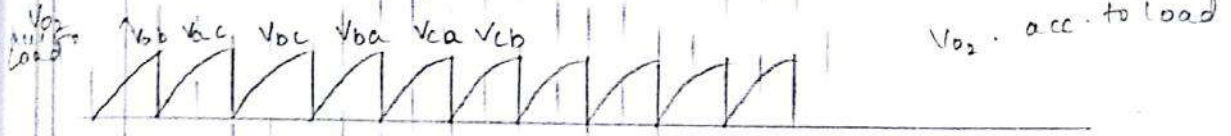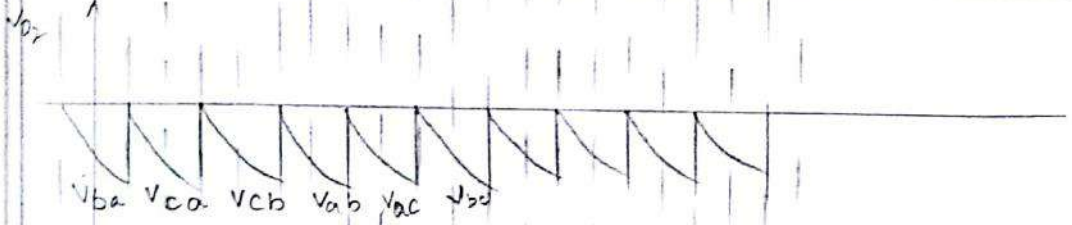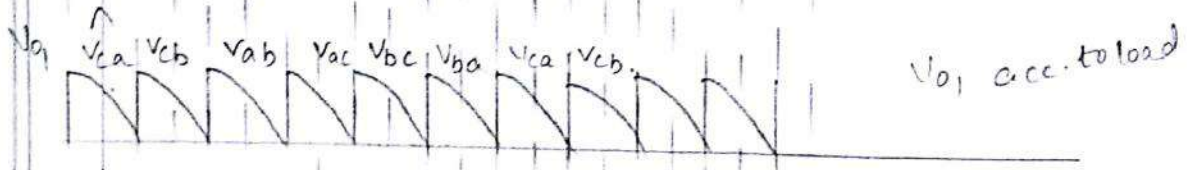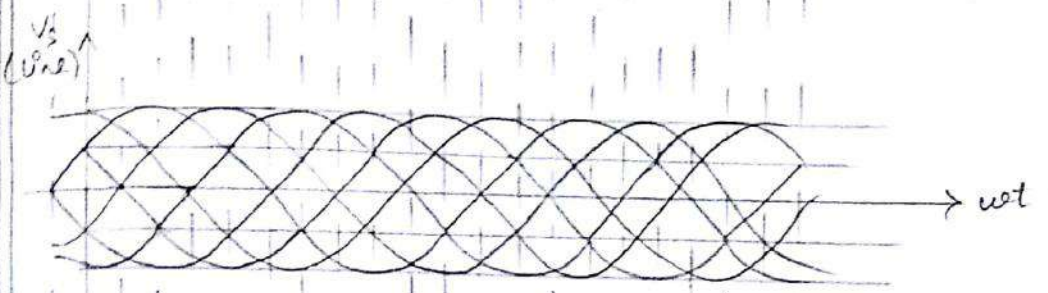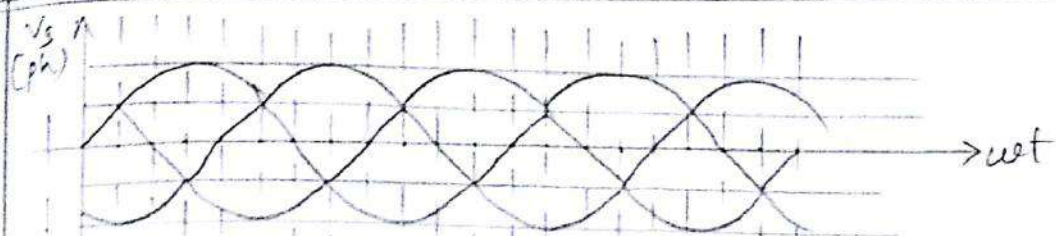
$90^\circ < \alpha_1 < 180^\circ \rightarrow$  Inverter  $\rightarrow -90^\circ < \alpha_2 < 180^\circ$



→ No load :

→  $I_o = 0$ , the converter carries the circulating current.

→ at load :

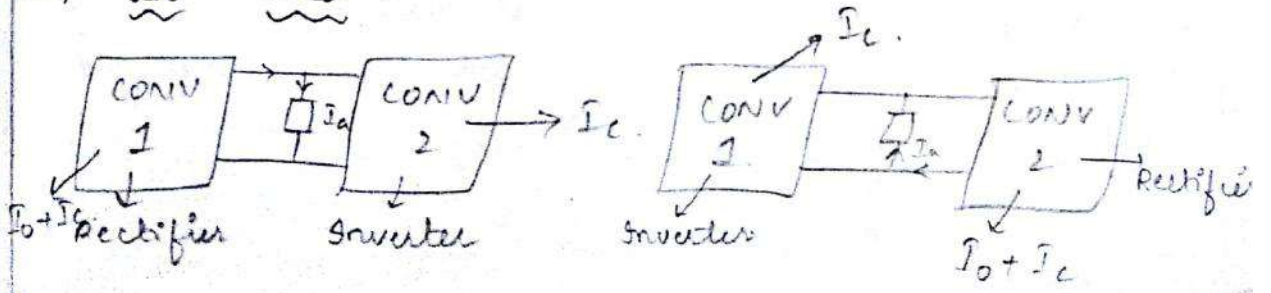




CHOPPER CONTROLLED DRIVES.

Based on their type of operation, there are four types of choppers.

1. Class - A.
2. Class - B
3. Class - C
4. class - D.

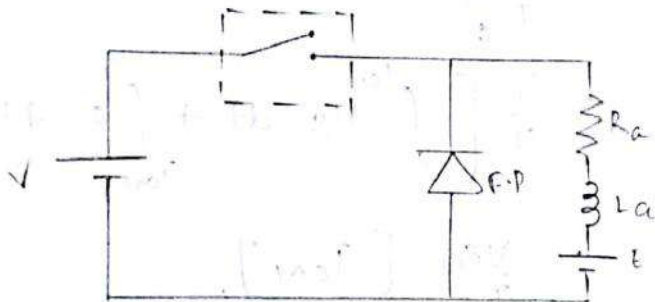1. FIRST QUADRANT CHOPPER (OR) CLASS - A CHOPPER: (Separately Excited motor)  
 → Continuous conduction mode.



During T<sub>ON</sub>:



$V_o = V_{in}.$

→ Inductor stores energy.

→ when switch is closed, F.D get open circuit & we get,  $V_o = V_{in}.$


During T<sub>OFF</sub>:



$V_o = 0.$

→ Inductor discharges.

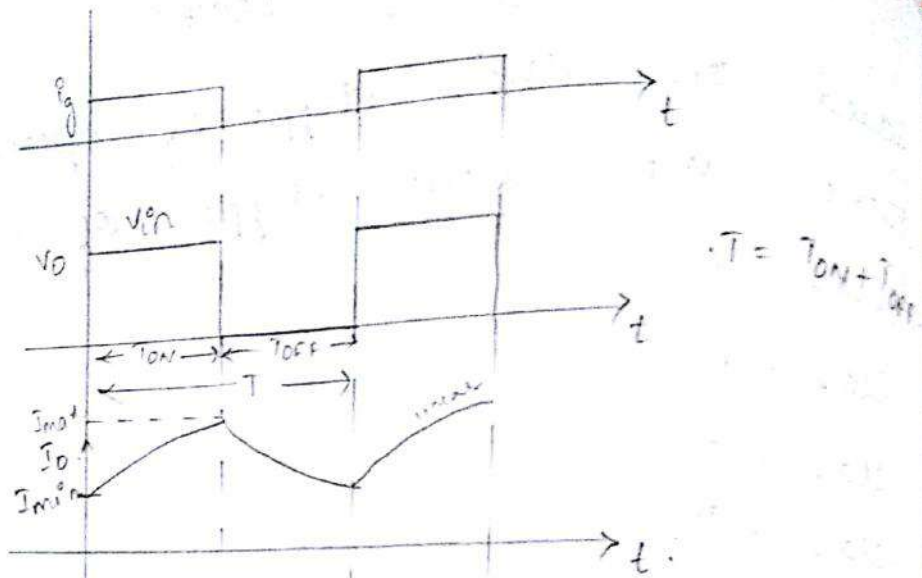→ when switch is open, F.D. get short circuited so, no current flow through it. so,  $V_o = 0.$



→ Average output voltage :

$$V_o = \frac{1}{T} \int_0^T f(t) dt$$

$$= \frac{1}{T} \left[ \int_0^{T_{ON}} V_{in} dt + \int_{T_{ON}}^T 0 \cdot dt \right]$$

$$= \frac{V_{in}}{T} [T_{ON}]$$


$$\therefore V_o = V_{in} \cdot \left[ \frac{T_{ON}}{T} \right]$$

Let, duty ratio,  $\delta = \frac{T_{ON}}{T}$


$$\text{Then, } V_o = \delta \cdot V_{in}$$

As  $T_{ON} \uparrow$ ,  $\delta \uparrow$ ,  $V_o \uparrow$ ,  $\omega_m \uparrow$ .


→ QUADRANT OF OPERATION :

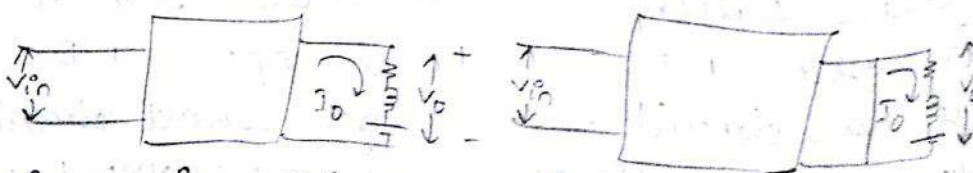

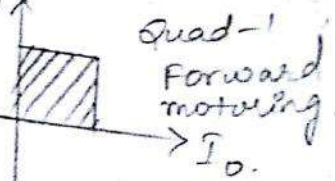By using this chopper, we get single quadrant operation.




Steady State Analysis:

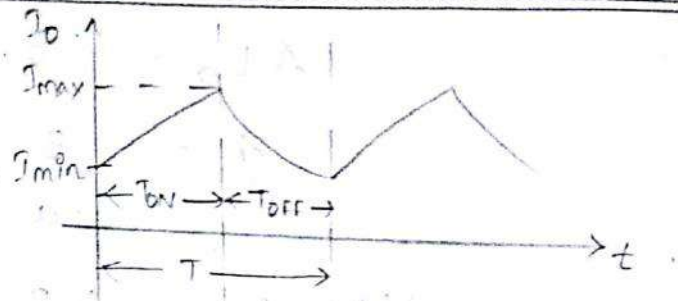

when,  $0 < t < T_{on}$

at  $t=0$ ,  $I(0) = I_{min}$ .

at  $t = T_{on}$ ,  $I(t) = I_{max}$ .

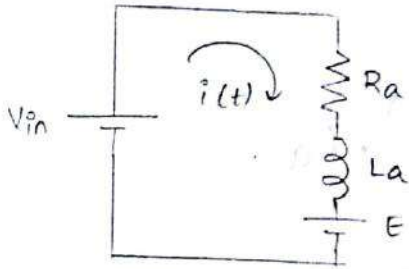

Applying KVL,

$$V_{in} = i(t) R_a + L_a \frac{di(t)}{dt} + E$$

$$\Rightarrow V_{in} - E = R_a i(t) + L_a \frac{di(t)}{dt}$$

Applying Laplace transform on both sides.

$$V_{in}/s - E/s = R_a I(s) + L_a [sI(s) - I(0)]$$

$$\frac{V_{in} - E}{s} = R_a I(s) + L_a [sI(s) - I_{min}]$$

$$\frac{V_{in} - E}{s} = (R_a + sL_a) I(s) - L_a I_{min}$$

$$\frac{V_{in} - E}{s} + L_a I_{min} = (R_a + sL_a) I(s)$$

$$\therefore I(s) = \frac{V_{in} - E}{s(R_a + sL_a)} + \frac{L_a I_{min}}{(R_a + sL_a)}$$

By using partial fractions,

$$\frac{V_{in} - E}{s(R_a + sL_a)} = \frac{A}{s} + \frac{B}{R_a + sL_a}$$

$$V_{in} - E = A(R_a + sL_a) + Bs$$

$$V_{in} - E = (AL + B)s + AR_a$$

Then,  $AL_a + B = 0$ .



$$A L_a = -B.$$

$$A = -\frac{B}{L_a}.$$

$$V_{in} - E = A R_a.$$

$$A = \frac{V_{in} - E}{R_a}.$$

$$B = -A L_a.$$

$$\therefore B = -\frac{(V_{in} - E) \cdot L_a}{R_a}.$$

$$\text{Then, } \frac{L_a I_{min}}{L_a \left(s + \frac{R_a}{L_a}\right)} = \frac{I_{min}}{\left(s + \frac{R_a}{L_a}\right)}.$$

$$\Rightarrow I(s) = \frac{V_{in} - E}{R_a} \left[ \frac{1}{s} - \frac{L_a}{R_a + s L_a} \right] + \frac{I_{min}}{\left(s + \frac{R_a}{L_a}\right)}$$

$$I(s) = \frac{V_{in} - E}{R_a} \left[ \frac{1}{s} - \frac{1}{\left(s + \frac{R_a}{L_a}\right)} \right] + \frac{I_{min}}{\left(s + \frac{R_a}{L_a}\right)}$$

$$\Rightarrow I(t) = \frac{V_{in} - E}{R_a} \left[ 1 - e^{-\left(\frac{R_a}{L_a}\right)t} \right] + I_{min} \cdot e^{-\left(\frac{R_a}{L_a}\right)t}$$

$$\text{Let } \tau = \frac{L_a}{R_a}.$$

$$\text{Then, } I(t) = \frac{V_{in} - E}{R_a} (1 - e^{-t/\tau}) + I_{min} \cdot e^{-t/\tau} \quad (1)$$

$$t = T_{ON}, \quad I(t) = I_{max}, \quad \text{for } 0 < t < T_{ON}.$$

$$I_{max} = \frac{V_{in} - E}{R_a} \left[ 1 - e^{-T_{ON}/\tau} \right] + I_{min} \cdot e^{-T_{ON}/\tau} \quad (2)$$

$$\text{when } T_{ON} < t < T.$$

$$0 < t - T_{ON} < T - T_{ON}.$$


$$\text{Let } t' = t - T_{ON}.$$

$$\Rightarrow 0 < t' < T - T_{ON}$$

$$\text{at } t' = 0, \quad I(t) = I_{max}$$

$$\text{at } t' = T - T_{ON}, \quad I(t) = I_{min}$$

$$I_0(R) + L \frac{dI}{dt} + E = 0$$

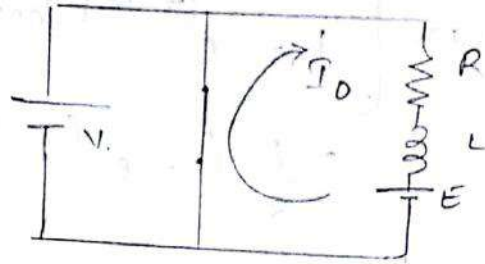

Apply Laplace

transform on both sides.

$$R I_0(s) + L [s I_0(s) - I_{max}] + \frac{E}{s} = 0$$

$$\Rightarrow I_0(s) [R + sL] = -\frac{E}{s} + L \cdot I_{max}$$

$$\therefore I_0(s) = \frac{-E}{s(R + sL)} + \frac{L \cdot I_{max}}{(R + sL)}$$

Then, using partial fractions,

$$I_0(s) = -\frac{E}{R} \left[ \frac{1}{s} - \frac{1}{(s + R/L)} \right] + \frac{I_{max}}{(s + R/L)}$$

Apply inverse Laplace on both sides.

$$I_0(t) = -\frac{E}{R} [1 - e^{-t/\tau}] + I_{max} \cdot e^{-t/\tau} \quad (3)$$

$$\text{where } \tau = \frac{L}{R}$$

$$\text{at } t' = T - T_{ON}, \quad I(t) = I_{min}$$

$$\therefore I_{min} = -\frac{E}{R} [1 - e^{-(T - T_{ON})/\tau}] + I_{max} \cdot e^{-(T - T_{ON})/\tau} \quad (4)$$

→ Substitute eq (4) in eq (2), we get

$$I_{max} = \frac{I_{min} - E}{R} [1 - e^{-T_{ON}/\tau}] + I_{min} \cdot e^{-T_{ON}/\tau}$$

$$\text{where, } I_{min} = -\frac{E}{R} [1 - e^{-(T - T_{ON})/\tau}] + I_{max} \cdot e^{-(T - T_{ON})/\tau}$$

$$\therefore I_{max} = \frac{V_{in} - E}{R} \left[ 1 - e^{-T_{on}/\tau} \right] \left[ \frac{E}{R} \left( 1 - e^{-(T-T_{on})/\tau} \right) \right]$$

$$I_{max} \left[ e^{-(T-T_{on})/\tau} \right] \cdot \left[ e^{-T_{on}/\tau} \right]$$

$$I_{max} \left[ 1 - e^{-(T+T_{on}-T_{on})/\tau} \right] = \frac{V_{in} - E}{R} \left[ 1 - e^{-T/\tau} \right]$$

$$- \frac{E}{R} \left( 1 - e^{-(T-T_{on})/\tau} \right) \cdot \left( e^{-T_{on}/\tau} \right)$$

$$I_{max} \left[ 1 - e^{-T/\tau} \right] = \frac{V_{in} - E}{R} \left[ 1 - e^{-T/\tau} \right]$$

$$- \frac{E}{R} \left[ e^{-T_{on}/\tau} - e^{-T/\tau} \right]$$

$$= \frac{V_{in}}{R} - \frac{V_{in}}{R} e^{-T_{on}/\tau} - \frac{E}{R} + \frac{E}{R} e^{-T_{on}/\tau}$$

$$- \frac{E}{R} e^{-T_{on}/\tau} + \frac{E}{R} e^{-T/\tau}$$

$$I_{max} = \frac{V_{in}}{R} \left[ 1 - e^{-T_{on}/\tau} \right] - \frac{E}{R} \left[ 1 - e^{-T/\tau} \right]$$

$$\therefore I_{max} = \frac{V_{in}}{R} \left[ \frac{1 - e^{-T_{on}/\tau}}{1 - e^{-T/\tau}} \right] - \frac{E}{R} \quad (5)$$

Substitute Eq (5) in Eq (4)

$$I_{min} = -\frac{E}{R} \left[ 1 - e^{-(T-T_{on})/\tau} \right] + I_{max} \cdot e^{-(T-T_{on})/\tau}$$

$$I_{min} = -\frac{E}{R} \left[ 1 - e^{-(T-T_{on})/\tau} \right] + \left[ \frac{V_{in}}{R} \left[ \frac{1 - e^{-T_{on}/\tau}}{1 - e^{-T/\tau}} \right] - \frac{E}{R} \right] \cdot e^{-(T-T_{on})/\tau}$$

$$I_{min} = -\frac{E}{R} \left[ 1 - e^{-(T-T_{on})/\tau} \right] + \frac{V_{in}}{R} \left[ \frac{1 - e^{-T_{on}/\tau}}{1 - e^{-T/\tau}} \right] \cdot e^{-(T-T_{on})/\tau}$$

$$- \frac{E}{R} \cdot e^{-(T-T_{on})/\tau}$$



$$I_{min} = -\frac{E}{R} \left[ 1 - e^{-(T-T_{ON})/\tau} + e^{-(T-T_{ON})/\tau} \right] + \frac{V_{in}}{R} \left[ \frac{1 - e^{-T_{ON}/\tau}}{1 - e^{-T/\tau}} \right] \cdot e^{-(T-T_{ON})/\tau}$$



$$I_{min} = -\frac{E}{R} + \frac{V_{in}}{R} \left[ \frac{1 - e^{-T_{ON}/\tau}}{1 - e^{-T/\tau}} \right] \cdot e^{-(T-T_{ON})/\tau}$$

$$= -\frac{E}{R} + \frac{V_{in}}{R} \cdot \left[ \frac{1 - e^{-T_{ON}/\tau}}{1 - e^{-T/\tau}} \right] \cdot \left[ \frac{e^{T_{ON}/\tau}}{e^{T/\tau}} \right]$$

$$\therefore I_{min} = -\frac{E}{R} + \frac{V_{in}}{R} \left[ \frac{e^{T_{ON}/\tau} - 1}{e^{T/\tau} - 1} \right] \quad \text{--- (6)}$$

Steady State Ripple :  $(I_{max} - I_{min})$ .
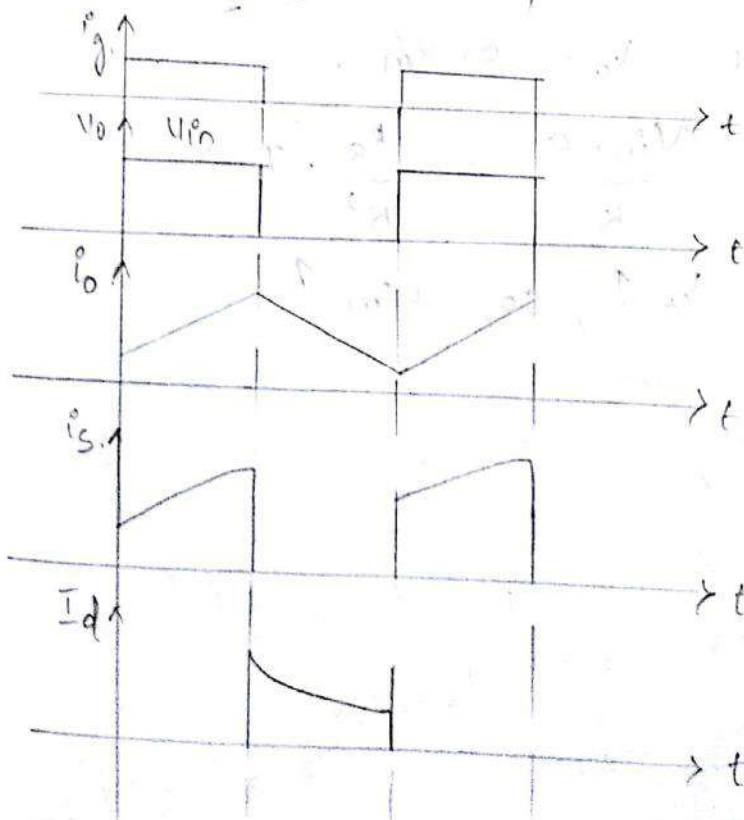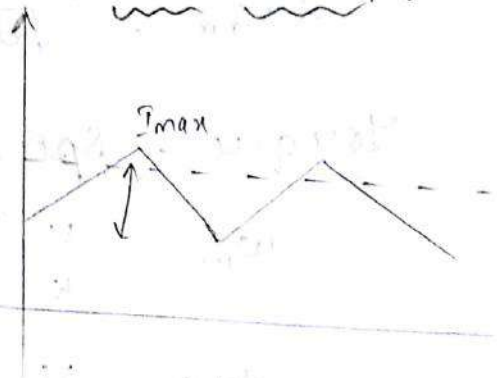
$$I_{max} - I_{min} = \frac{V_{in}}{R} \left[ \frac{1 - e^{-T_{ON}/\tau}}{1 - e^{-T/\tau}} \right] - \frac{E}{R} + \frac{E}{R} - \frac{V_{in}}{R} \left[ \frac{e^{T_{ON}/\tau} - 1}{e^{T/\tau} - 1} \right]$$



$$V_0 = \delta \cdot V_m$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_m^2 dt}$$

$$= \sqrt{\frac{V_m^2}{T} \int_0^{T_{ON}} i \cdot dt}$$

$$= \sqrt{V_m^2 \cdot \frac{T_{ON}}{T}}$$

$$= V_m \sqrt{\frac{T_{ON}}{T}}$$

$$V_{rms} = \sqrt{\delta} \cdot V_m$$

Torque - Speed characteristics:

$$\omega_m = \frac{V}{K} - \frac{R_a \cdot T}{K^2}$$


Here,  $V = V_0$ .

where,  $V_0 = \delta \cdot V_m$ .


$$\therefore \omega_m = \frac{V_m \cdot \delta}{K} - \frac{R_a \cdot T}{K^2}$$

As  $\delta \uparrow$ ,  $V_0 \uparrow$ , so,  $\omega_m \uparrow$ .

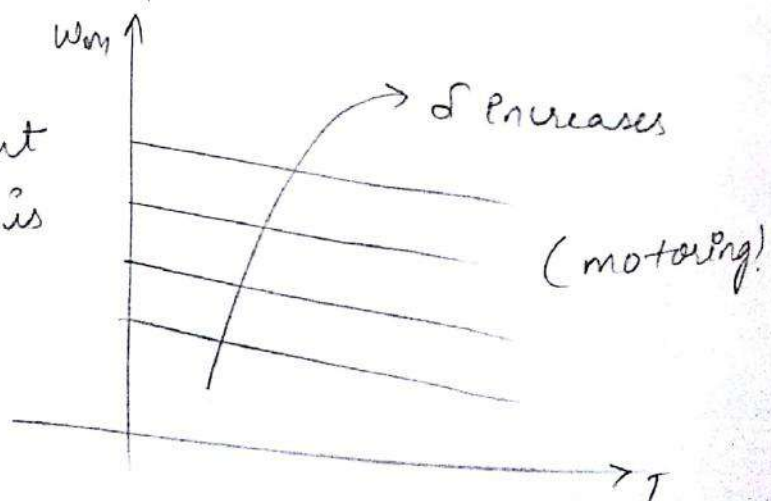Since, it is separately excited / shunt motor,  $\phi$  is constant



## \* SERIES MOTOR :-

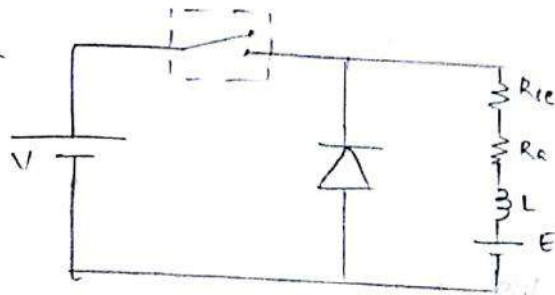


## Torque - Speed characteristics :-

$$\omega_m = \frac{V_0}{\sqrt{k_e k_f} \sqrt{T}} - \frac{R_a + R_{se}}{k_e k_f}$$

$$\therefore \omega_m = \frac{V_{in} \cdot \delta}{\sqrt{k_e k_f} \sqrt{T}} - \frac{R_a + R_{se}}{k_e k_f}$$

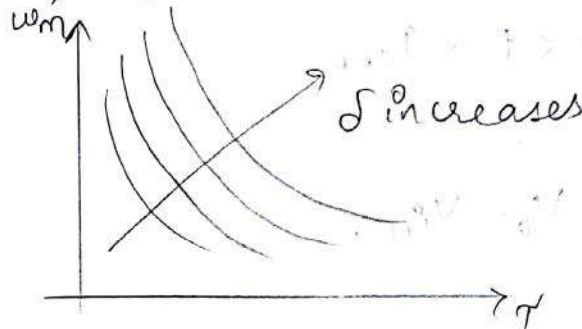As  $\delta \uparrow$ ,  $V_0 \uparrow$ ,  $\omega_m \uparrow$ .



## REGENERATIVE BRAKING CONTROL USING CHOPPERS:


1) Braking

2) Power from load to source.

\* we need to change the direction of current.

\* Fed back to the supply.



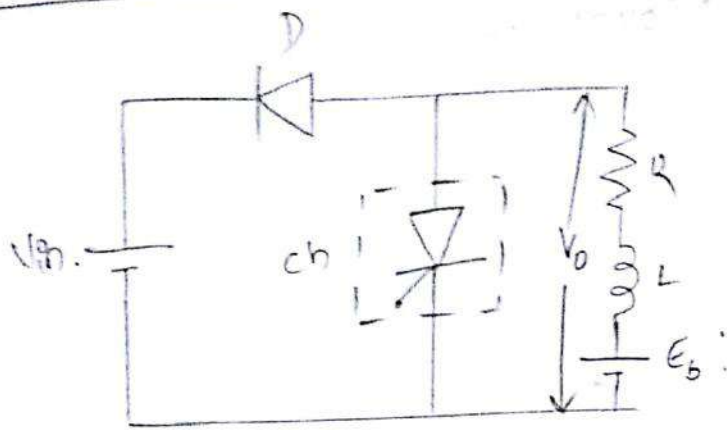


when  $E > V_{in}$  :

→  $0 < t < T_{on}$ .

\*  $T_{on}$  :-

→ a part of energy is dissipated in  $R_a$  & stored in inductor.



∴  $V_o = 0$ .

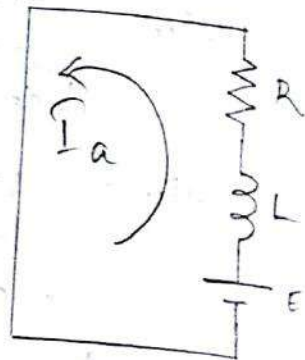

→  $T_{on} < t < T_{off}$ .

\*  $T_{off}$  :-

Then,  $V_o = V_{in}$ .

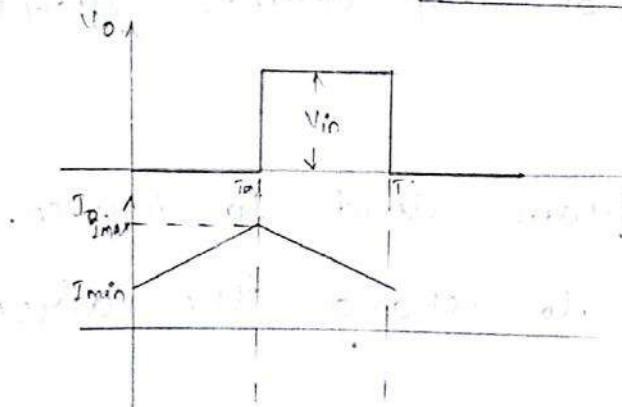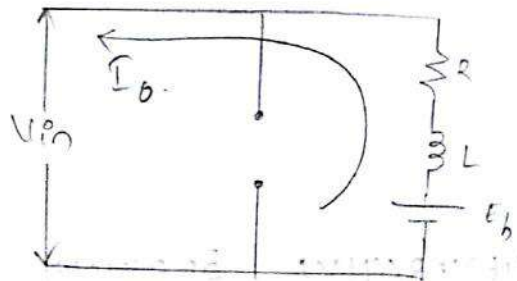

\* average output voltage :

$$V_o(\text{avg}) = \frac{1}{T} \int_0^T f(t) dt.$$

$$= \frac{1}{T} \int_{T_{on}}^T V_{in} dt.$$

$$= \frac{V_{in}}{T} [T - T_{ON}]$$

$$\therefore V_o(\text{avg}) = V_{in} \left[ 1 - \frac{T_{ON}}{T} \right]$$

$$\Rightarrow \boxed{V_o(\text{avg}) = V_{in} (1 - \delta)}$$


$$* V_{rms} = \sqrt{\frac{1}{T} \int_0^T [f(t)]^2 dt}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_{T_{ON}}^T V_{in}^2 dt}$$


$$V_{rms} = \sqrt{\frac{V_{in}^2}{T} [T - T_{ON}]}$$

$$\therefore \boxed{V_{rms} = V_{in} \sqrt{1 - \delta}}$$


→ QUADRANT OF OPERATION:

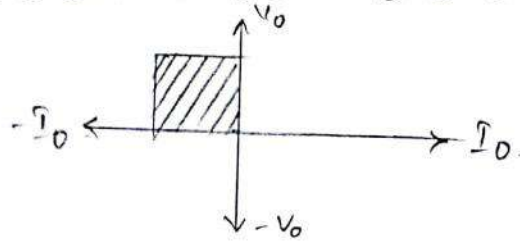


for  $0 < t < T_{ON}$ :

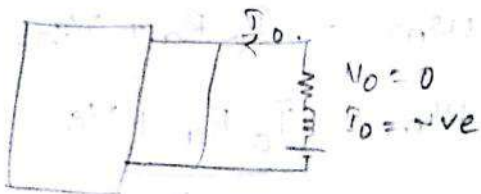


for  $T_{ON} < t < T$ :

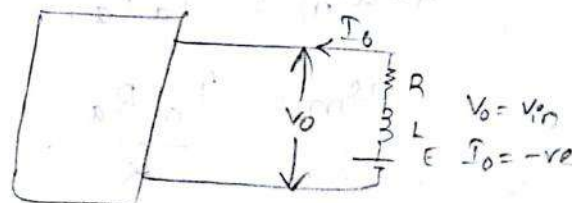

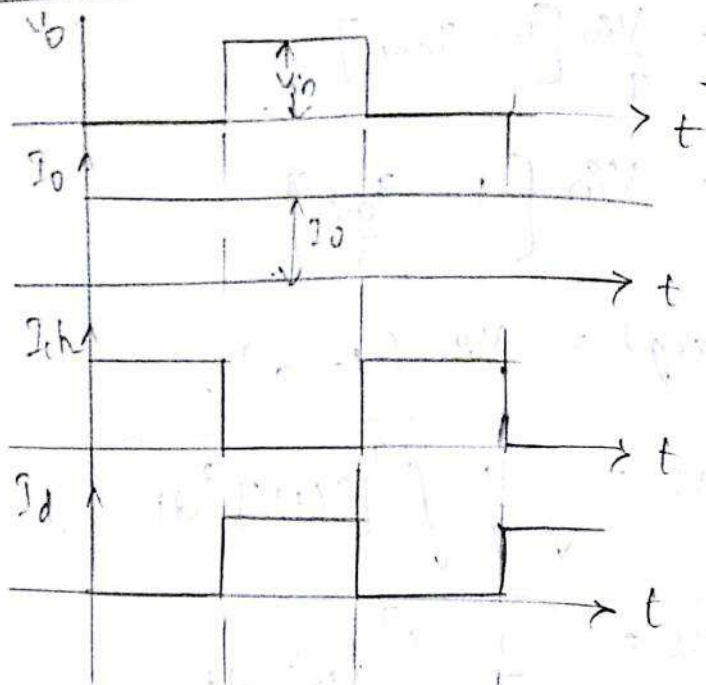

\* Maximum and Minimum Braking Speeds:

$0 < t < T_{ON}$  :

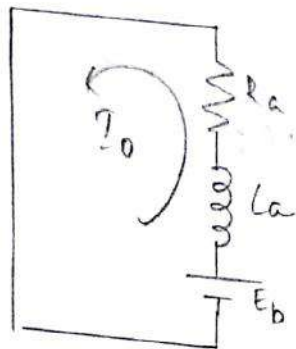


$$E = I_a R_a$$

$$K \cdot \omega_m = I_a R_a$$

$$\omega_m = \frac{I_a R_a}{K}$$

Minimum Braking Speed.

$T_{ON} < t < T$  :

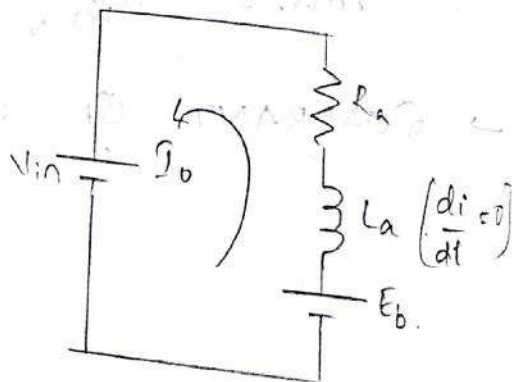

$$E = I_a R_a + V_{in}$$

$$K \cdot \omega_m = I_a R_a + V_{in}$$

$$\omega_m = \frac{I_a R_a + V_{in}}{K}$$

Maximum Braking Speed.



## Speed - Torque characteristics :

→ Basic Equation is  $E_b = I_a R_a + V$ .

$$\text{Torque } T = -k_e \phi I_a.$$

$$\therefore E_b = k_e \phi \omega_m.$$

$$E = I_a R_a + V.$$

$$k_e \phi \omega_m = I_a R_a + V.$$

$$\text{where, } I_a = \frac{-T}{k_e \phi}.$$

$$\therefore k_e \phi \omega_m = \frac{-T}{k_e \phi} R_a + V.$$

$$\Rightarrow \omega_m = \frac{-T}{(k_e \phi)^2} R_a + \frac{V}{k_e \phi}.$$

Since  $\phi$  is constant,  $k = k_e \phi$ .


$$\therefore \omega_m = \frac{V}{k} - \frac{T}{k^2} R_a.$$

$$\text{where, } V = V_0.$$

$$\Rightarrow V_0 = V_{in} (1 - \delta).$$


$$\Rightarrow \omega_m = \frac{V_{in} (1 - \delta)}{k} - \frac{T}{k^2} R_a.$$

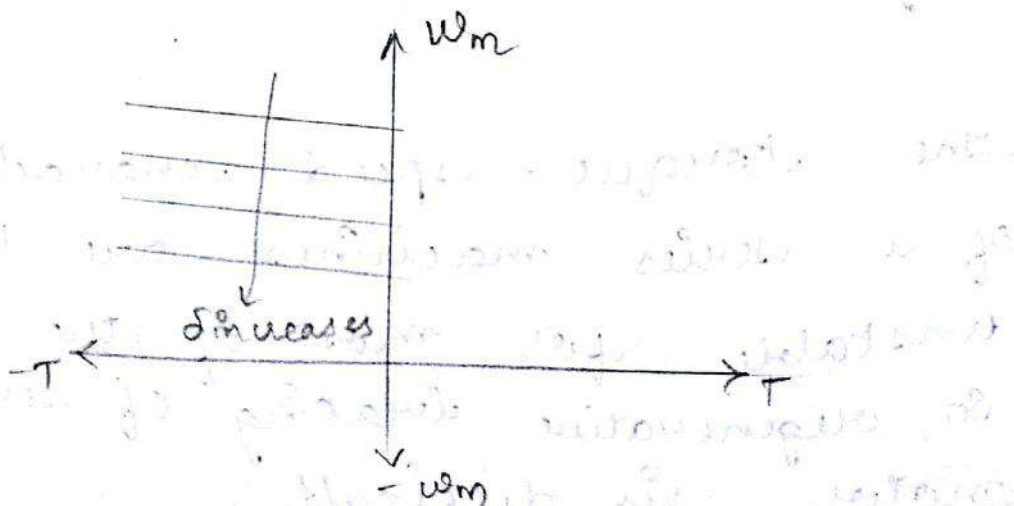As  $\delta \uparrow$ ,  $V_0 \downarrow$ ,  $\omega_m \downarrow$ .




57/1/16

SERIES MOTOR:

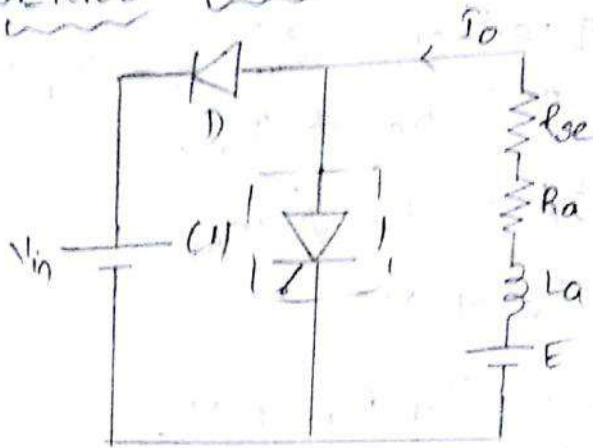

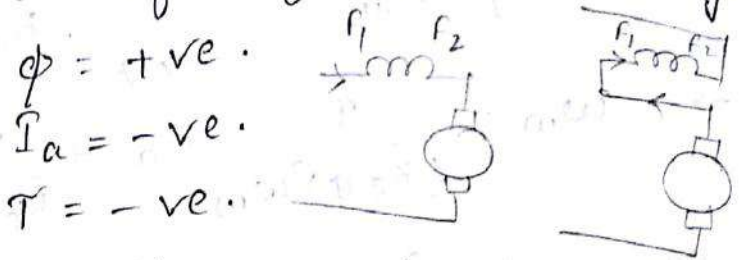→ we need to change the terminals of field windings



Basic equations:

$$E = V + I_a (R_a + R_{se})$$

$$T = -k_e k_f I_a^2$$

$$E = k_e \phi \omega_m$$

Then,  $k_e \phi \omega_m = V + I_a (R_a + R_{se})$


$$k_e \phi \omega_m = V + \sqrt{\frac{-T}{k_e k_f}} (R_a + R_{se})$$

$$\omega_m = \frac{V}{k_e \phi} + \sqrt{\frac{-T}{k_e k_f}} \cdot \frac{(R_a + R_{se})}{k_e \phi}$$


$$\therefore \omega_m = \frac{V}{k_e k_f I_a} + \sqrt{\frac{-T}{k_e k_f}} \cdot \frac{(R_a + R_{se})}{k_e k_f I_a}$$

The torque-speed characteristics of a series machines are highly unstable for most of the load. So, regenerative braking of series motor is difficult.
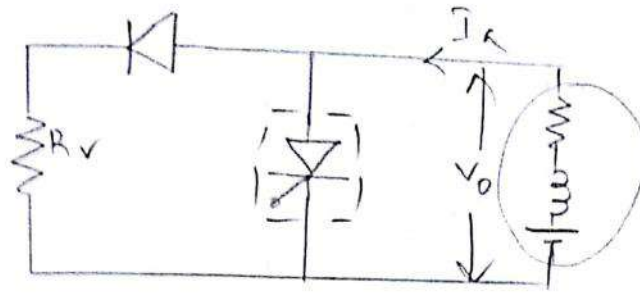
# DYNAMIC BRAKING CONTROL USING CHOPPERS:



During  $T_{ON}$ :

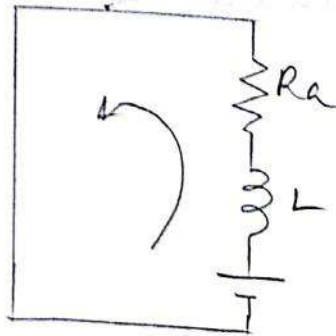

→ Inductor gets charged

→  $V_o = 0$ ,  $I_a = -ve$ .

\* Energy dissipated in the load,

$$E_b = I_a^2 R_a (T - T_{ON})$$

Average power dissipated during the interval  $T$ :


$$P_{avg} = \frac{E}{T} = \frac{I_a^2 R_a (T - T_{ON})}{T}$$

$$P_{avg} = I_a^2 R_a \left[ 1 - \frac{T_{ON}}{T} \right]$$


$$\therefore P_{avg} = I_a^2 R_a (1 - \delta)$$
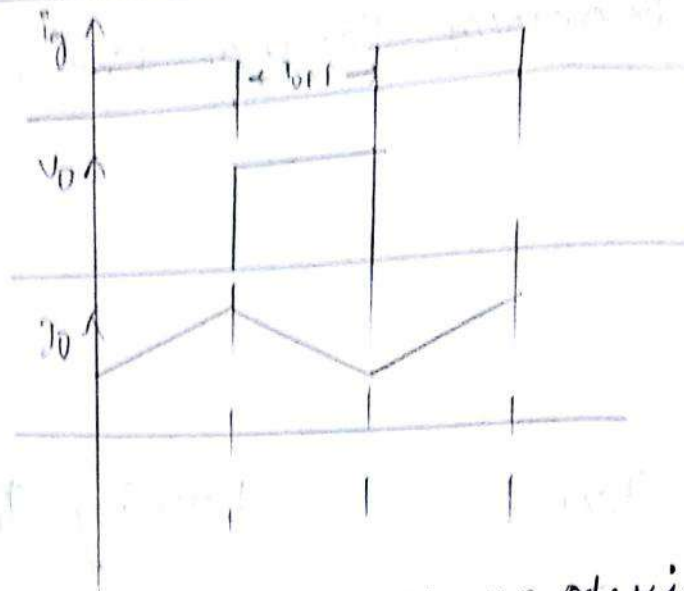
$$\Rightarrow \boxed{R_{eff} = R_a (1 - \delta)}$$






Torque-Speed characteristics:-

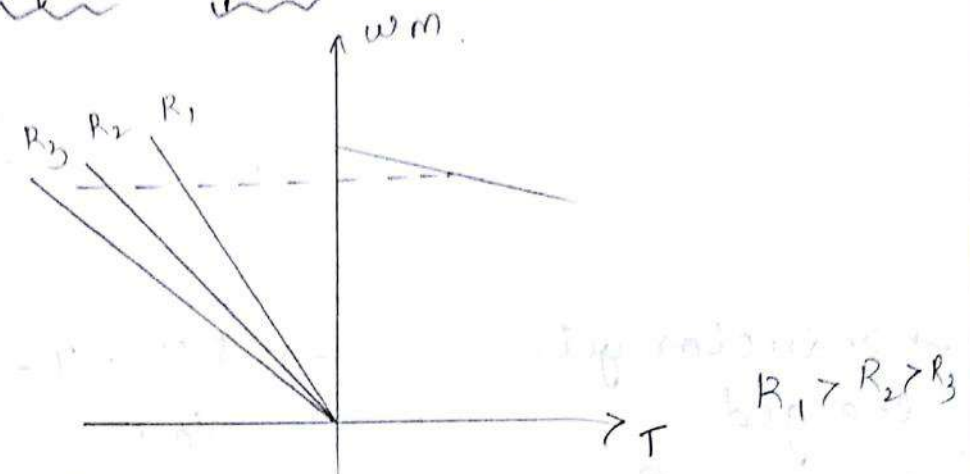

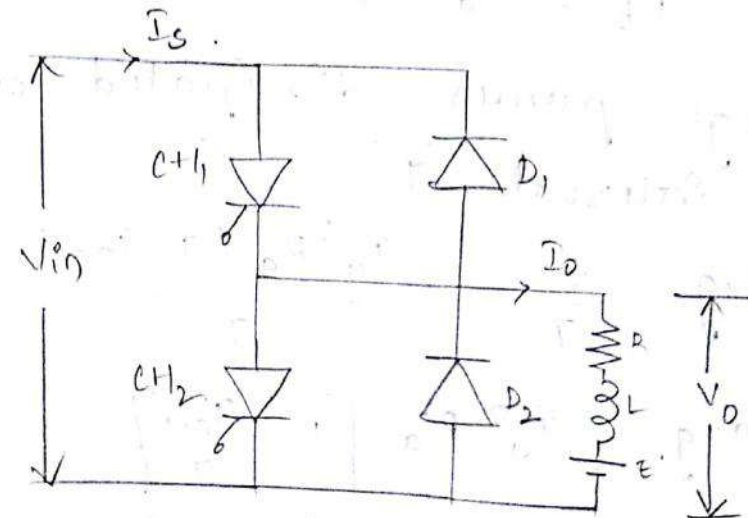→ TWO QUADRANT CHOPPER (OR)  
TYPE - C CHOPPER :-




1) 1<sup>st</sup> Quadrant operation (Motoring) :-

i)  $CH_1 \rightarrow ON$  ( $T_{ON}$ ).  $I_a = \frac{\delta V_{in} - E}{R_a}$  if  $\delta > E/V_{in}$ ,  $I_a = +ve$  (Motoring mode)

$V_o = V_{in}$

$I_o = +ve$

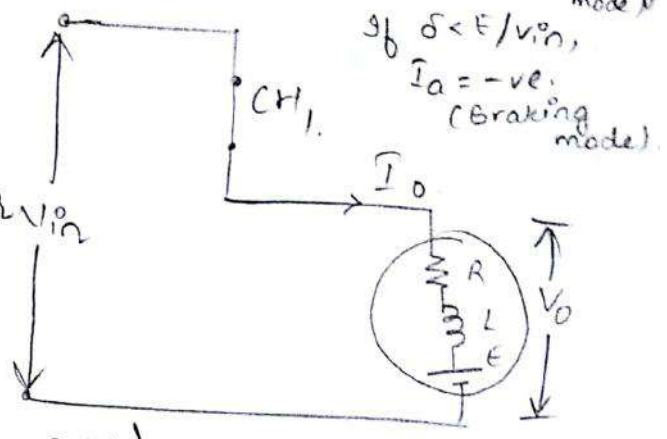$\rightarrow$  Inductor in motor gets charged.




ii)  $CH_1 \rightarrow OFF$  ( $D_2 ON$ ).

$V_o = 0$

$I_o = +ve$

$\rightarrow$  Inductor gets discharged.

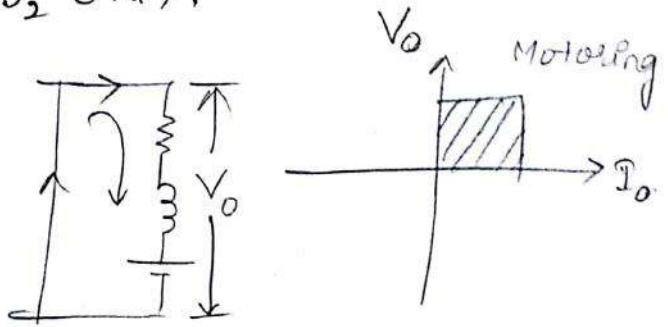

[Motoring controlling switch  $CH_1$ ].


2) 2<sup>nd</sup> Quadrant Operation (Braking) :-

i)  $CH_2 \rightarrow ON$ .

$\rightarrow$  The inductor charges.

$V_o = 0$



$I_o = -ve$

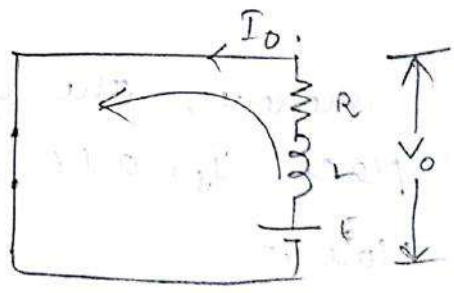


ii)  $CH_2 \rightarrow OFF$  ( $D_1$  is ON) :-

$V_o = V_{in}$


Req.  $\frac{1}{2} V_o = -ve$   
Braking

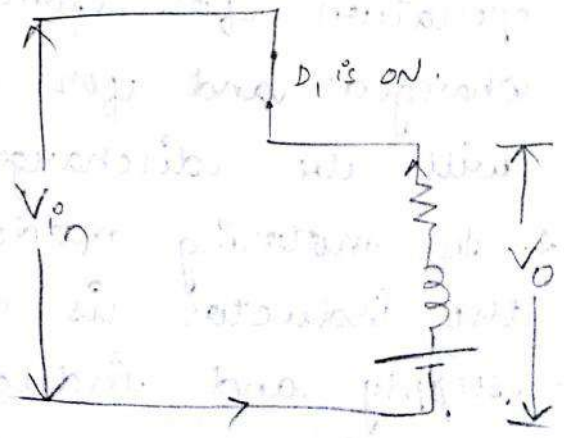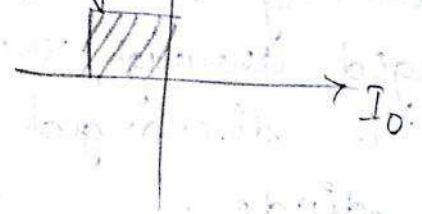

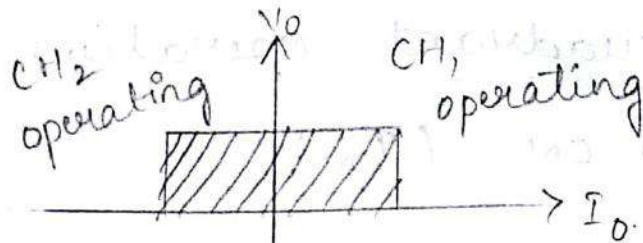

$$V_o = \delta V_{in} \Rightarrow 1) V = E + I_a R_a \therefore I_a = \frac{V - E}{R_a} = \frac{V_o - E}{R_a}$$

$$I_a = \frac{\delta V_{in} - E}{R_a}$$

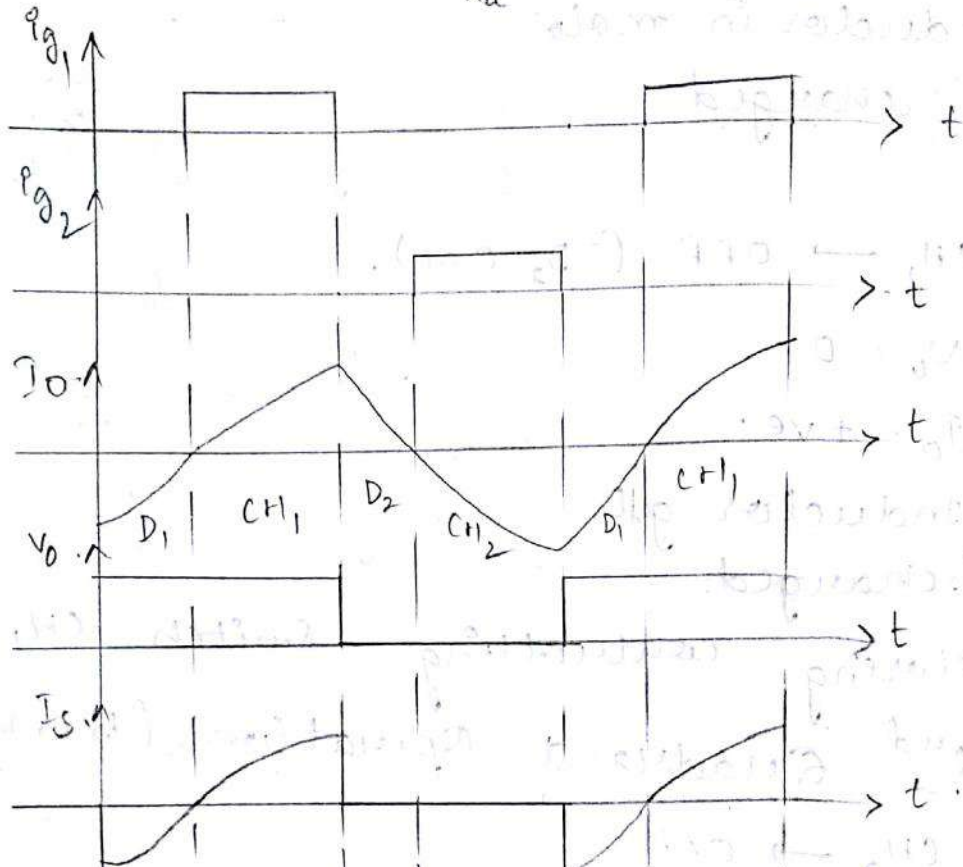

whenever the freewheeling action takes place  $I_s = 0$  i.e., when  $D_2$  is ON!



Note :-

1. In any quadrant or mode of operation for sometime inductor will be charged and for remaining time inductor will be discharged.
2. In motoring mode, during sometime the inductor is charged through the supply and inductor is discharged through free wheeling diode.



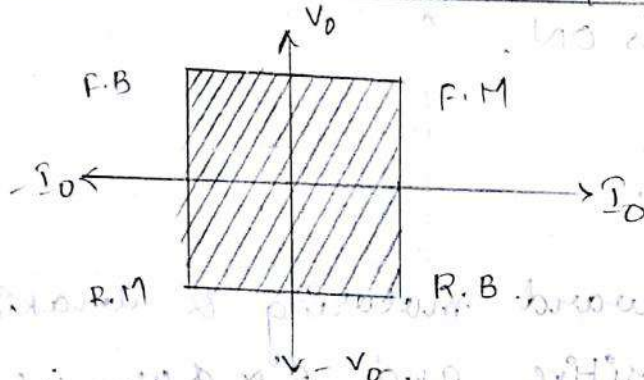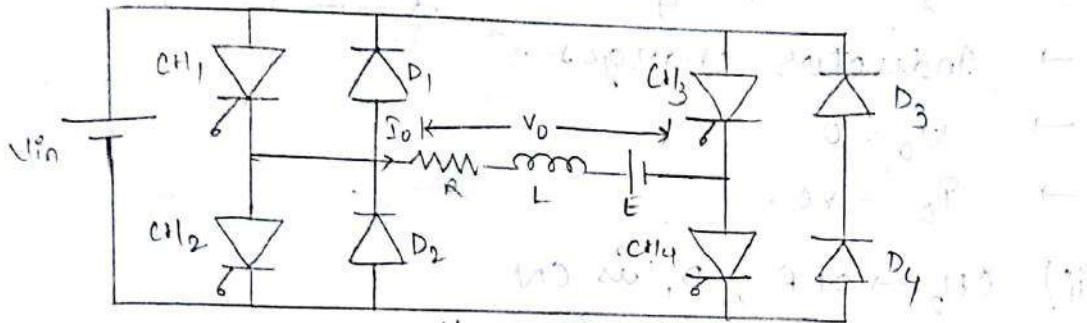
3. In braking operation, during sometime, the inductor is charged through back emf  $E_b$ , for the other time, inductor is discharged and gives back power to supply

→ FOUR QUADRANT OPERATION OF DRIVE USING CHOPPERS:



\* 1st QUADRANT OPERATION:


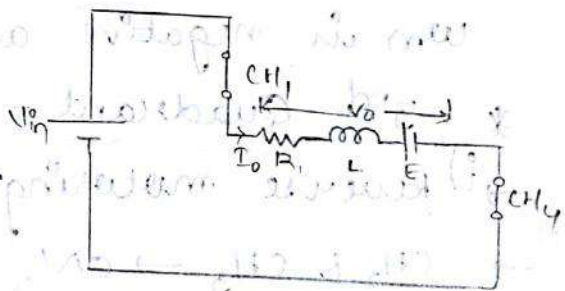
- i) → Forward Motoring.
- CH<sub>1</sub> & CH<sub>4</sub> are ON.
- Inductor gets charges.
- $V_o = V_{in}$ .
- $I_o$  is +ve.



- ii) → CH<sub>1</sub> is OFF, CH<sub>4</sub> is conducting

∴ D<sub>2</sub> is ON.

- $V_o = 0$ .
- $I_o = +ve$ .

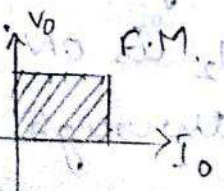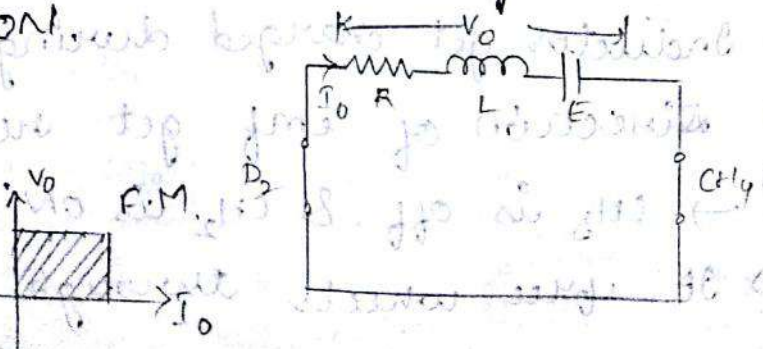


## \* 2nd Quadrant Operation:

→ Forward Braking.

→  $I_0$  has to change the direction.

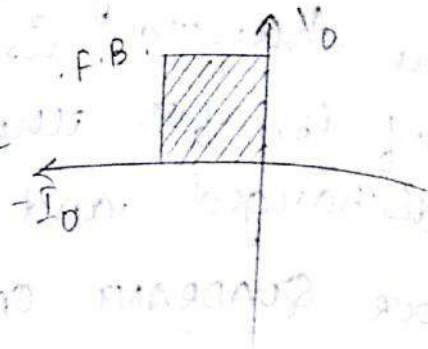→  $E$  should be greater than  $V$  [ $i.e., E > V$ ].




i)  $CH_2 \rightarrow ON$ ;  $D_4 \rightarrow ON$ .

→ Inductor charges.

→  $V_o = 0$ .


→  $I_0 = -ve$ .

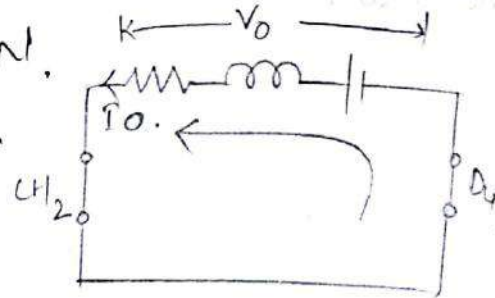

ii)  $CH_2 \rightarrow OFF$ ;  $D_1$  is ON  
&  $D_4$  is ON.

→  $V_o = V_{in}$ .

→  $I_0 = -ve$ .

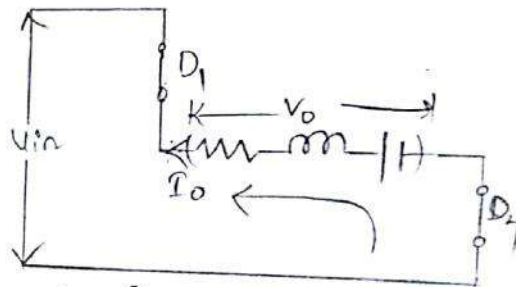

\* For forward motoring & braking speed,  $\omega_m$  is positive and  $E \propto \phi \omega_m$  i.e.,  $E = +ve$

\* For reverse motoring & braking speed,  $\omega_m$  is negative and  $E \propto -\phi \omega_m$  i.e.,  $E = -ve$ .

## \* 3rd Quadrant Operation:

→ i) Reverse motoring.

→  $CH_2$  &  $CH_3 \rightarrow ON$ .

→  $V_o = -V_{in}$


→  $I_0 = -ve$ .

→ Inductor get charged during this instant.

→ Direction of emf get reversed.

ii) →  $CH_3$  is off, &  $CH_2$  is ON.

→ It will wheel through diode  $D_4$ .


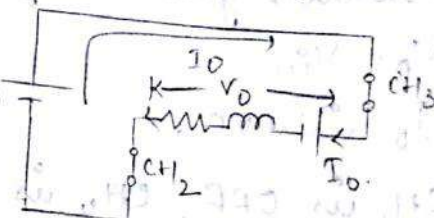




→ Inductor discharges.

→  $V_o = 0$ .

→  $I_o = -ve$ .

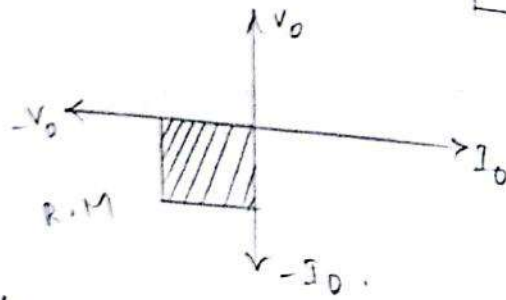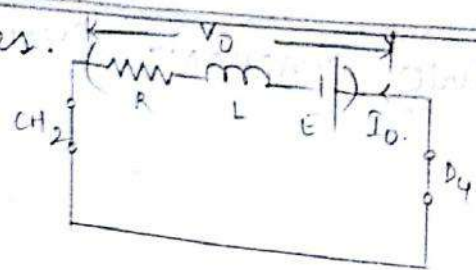

\* 4<sup>th</sup> Quadrant Operation:


→ i) Reverse Braking.

→  $CH_4$  is ON &  $D_2$  is ON.

→  $V_o = 0$ .

→  $I_o = +ve$ .

→ Inductor charges.

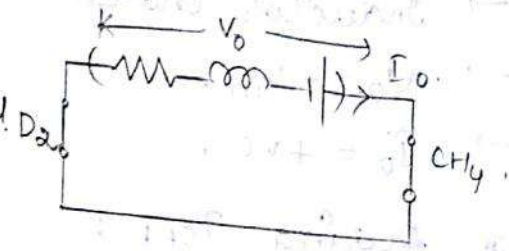



ii) →  $CH_4$  is OFF.

→ Inductor discharges

→  $V_o = -V_{in}$ .

→  $I_o = +ve$ .

→ Here,  $D_2$  &  $D_3$  → ON.

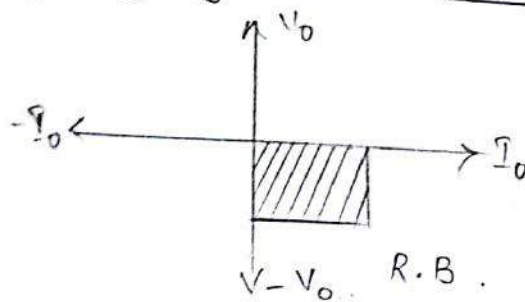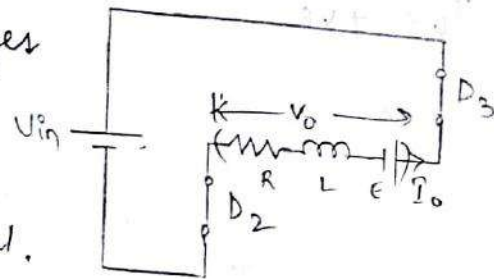


Quad 1	$CH_1 - CH_4$	$CH_4 - D_2$	$V_o = +ve$ $I_o = +ve$	(FM)
Quad 2	$CH_2 - D_4$	$D_1 - D_4$	$V_o = +ve$ $I_o = -ve$	(FB)
Quad 3	$CH_3 - CH_2$	$CH_2 - D_4$	$V_o = -ve$ $I_o = -ve$	(RM)
Quad 4	$CH_4 - D_2$	$D_2 - D_3$	$V_o = -ve$ $I_o = +ve$	(RB)

Inductor charges


Inductor discharges




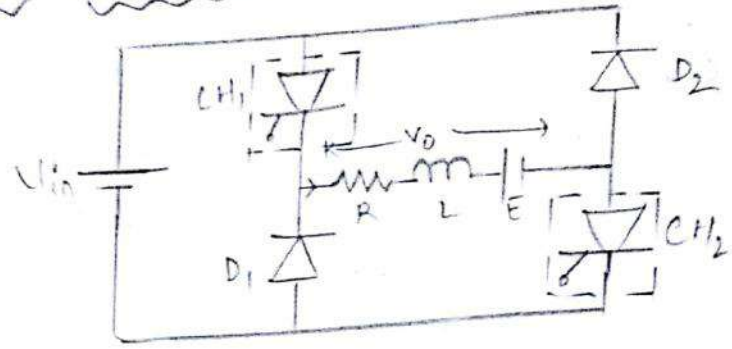
# TWO QUADRANT CHOPPER (OR) CLASS-D CHOPPER



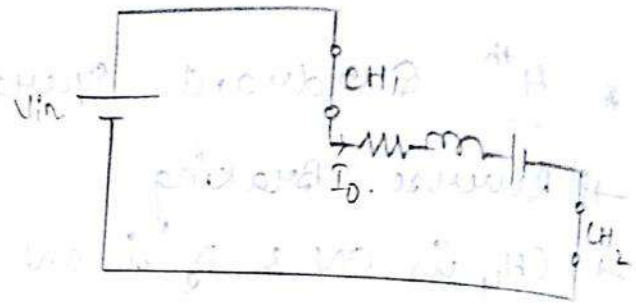- \* During  $T_{ON}$ :
- $CH_1$  &  $CH_2$  is ON.
  - Inductor charges
  - $V_o = +V_{in}$ .
  - $I_o = +ve$ .



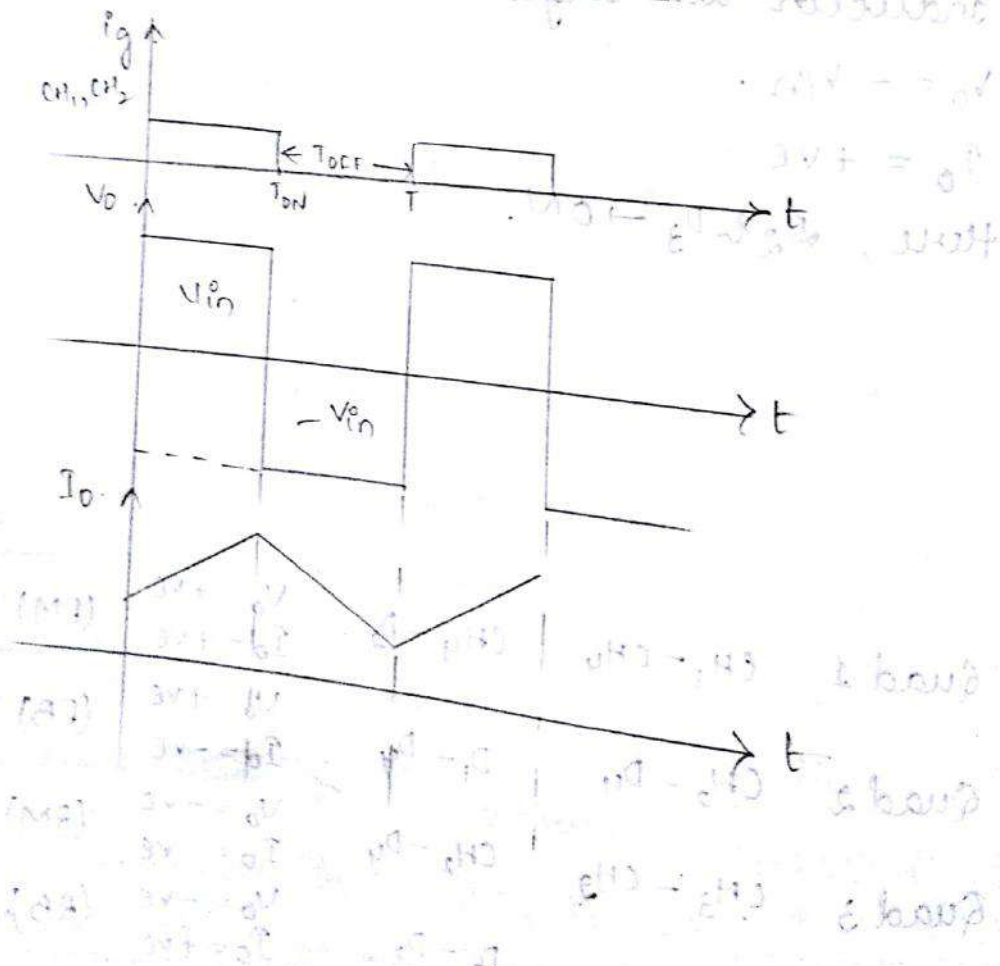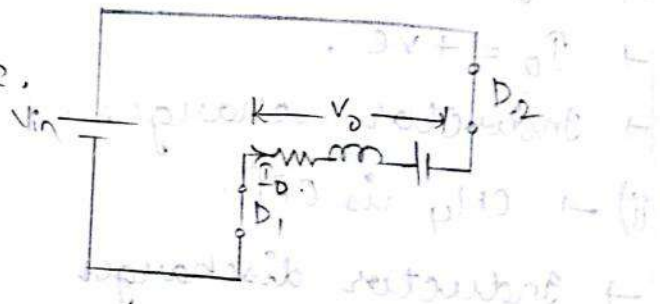
- \* During  $T_{OFF}$ :
- $CH_1$  &  $CH_2$  is OFF.
  - $V_o = -V_{in}$ .
  - $I_o = +ve$ .




\* 1st Quadrant Operation :-

$V_o = +V_{in}$  [Average should be +ve],  
 $I_o = +ve$

i)  $T_{ON} > T_{OFF}$  :-

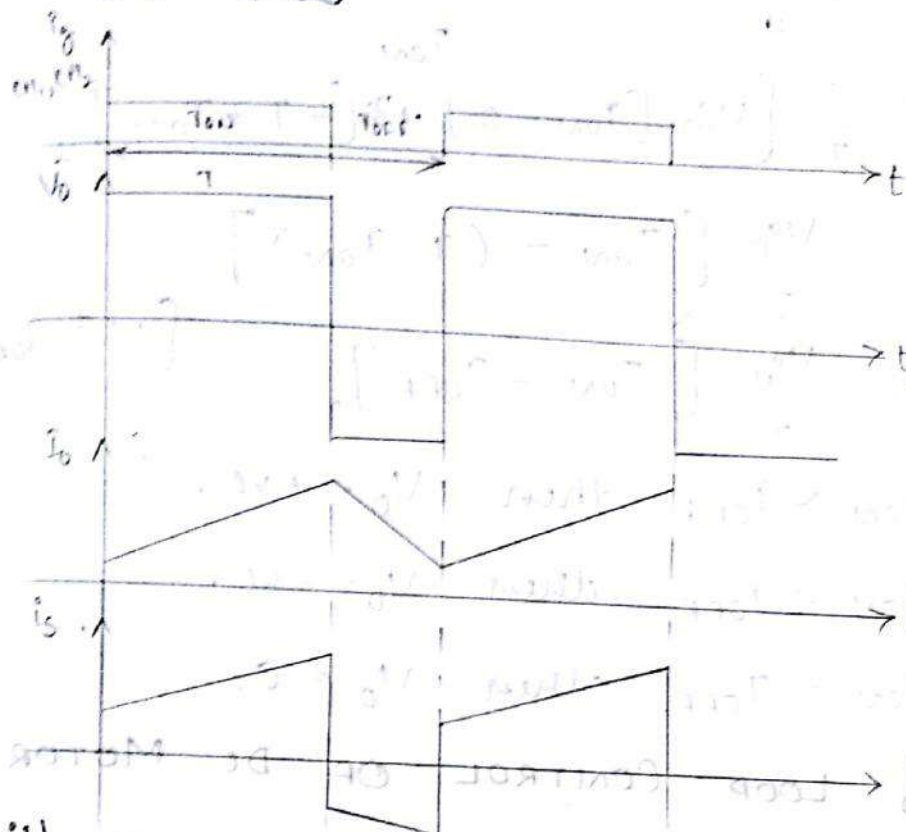

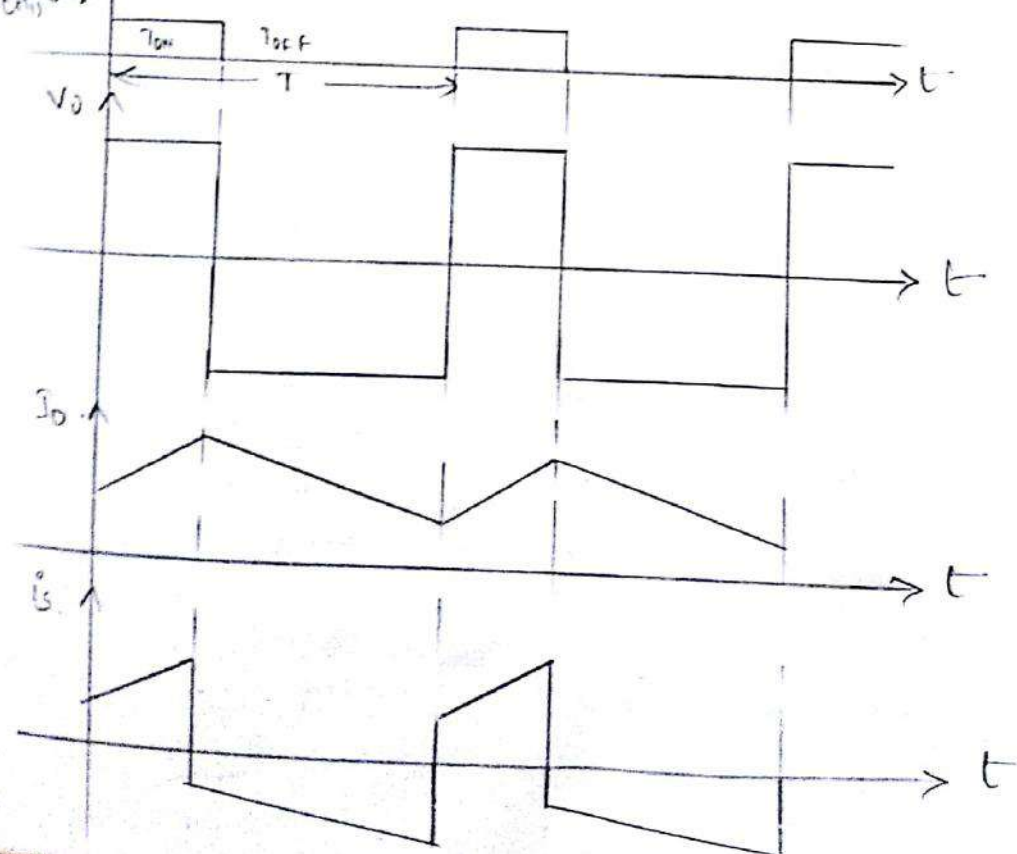ii)  $T_{OFF} > T_{ON}$  :-  $V_o = -ve$  ;  $I_o = +ve$  . [Avg  $\rightarrow -ve$ ]



Average output voltage,

$$V_o = \frac{1}{T} \int_0^T f(t) dt$$

$$V_o = \frac{1}{T} \int_0^{T_{ON}} V_{in} dt + \int_{T_{ON}}^T -V_{in} dt$$

$$V_o = \frac{1}{T} [V_{in} [T_{ON} - 0] + V_{in} [-T + T_{ON}]]$$

$$V_o = \frac{V_{in}}{T} [T_{ON} - (T - T_{ON})]$$

$$V_o = \frac{V_{in}}{T} [T_{ON} - T_{OFF}]$$


[ $\because T - T_{ON} = T_{OFF}$ ]

- \* If  $T_{ON} > T_{OFF}$  then  $V_o = +ve$ .
- \* If  $T_{ON} < T_{OFF}$  then  $V_o = -ve$ .
- \* If  $T_{ON} = T_{OFF}$  then  $V_o = 0$ .


7/1/15  
\*

CLOSED LOOP CONTROL OF DC MOTOR :



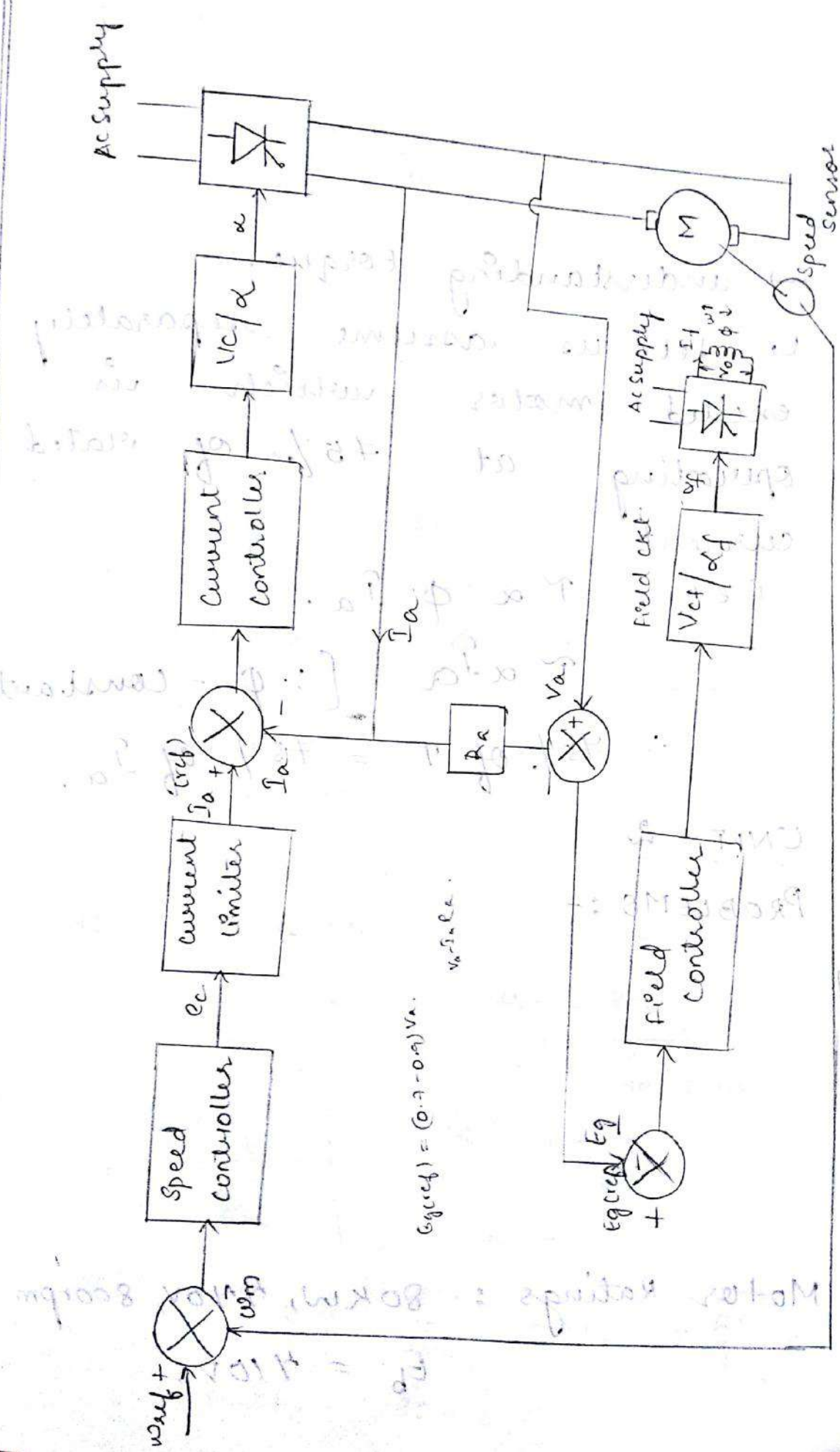

07/02/16

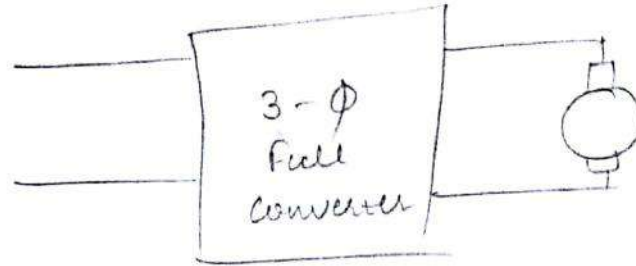

$$V_o = \frac{3V_{ml} \cos \alpha}{\pi}$$

↳ understanding torque.

↳ Let us assume separately excited motor which is operating at 75% of rated current.

i.e.,  $T \propto \phi I_a$ .


$$T \propto I_a \quad [\because \phi - \text{constant}]$$

$$\therefore 75\% \text{ of } T = 75\% \text{ of } I_a.$$

UNIT - 2

PROBLEMS :-

1.60

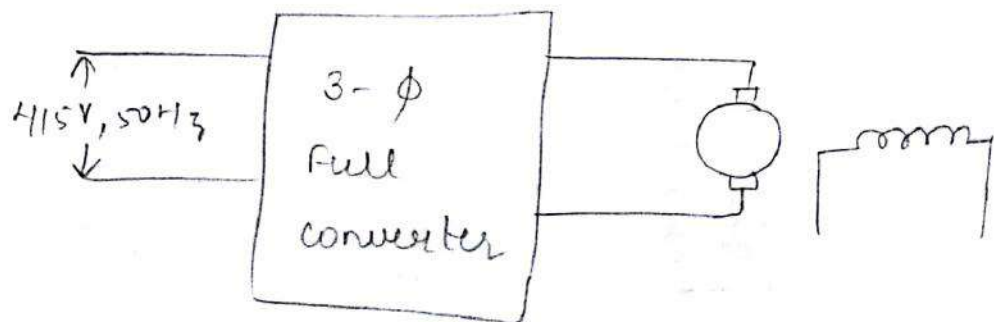


Motor Ratings : 80 kW, 440V, 800rpm

$$E_b = 410V.$$

$$I_a = \frac{P}{V}$$

$$I_a = \frac{80 \times 10^3}{440}$$

$$\therefore I_a = 181.81 \text{ A}$$

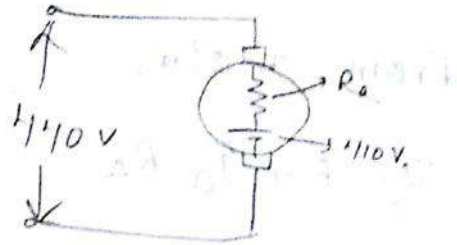

Then,  $V = E + I_a R_a$

$$440 = 410 + (181.81) R_a$$

$$30 = 181.81 R_a$$

$$\Rightarrow R_a = 0.165 \Omega$$

→ Operating Condition :-


Motor is operated at 600 rpm.

75% of rated torque.

$$= 75\% \text{ of } I_a$$

$$= 0.75 (181.81)$$

$$= 136.35 \text{ Amps}$$

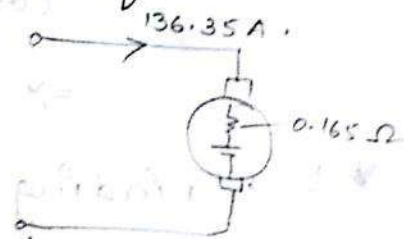

As  $E_b \propto \omega_m$

$E_{b1} = 410 \text{ V at } \omega_{m1} = 800 \text{ rpm}$

$E_{b2} = ? \text{ at } \omega_{m2} = 600 \text{ rpm}$

$$\frac{E_{b1}}{E_{b2}} = \frac{\omega_{m1}}{\omega_{m2}}$$


$$E_{b2} = \frac{\omega_{m2}}{\omega_{m1}} \times E_{b1} = \frac{600}{800} \times 410$$

$$\therefore E_{b2} = 307.5 \text{ V}$$



From motor,

$$V_o = E + I_a R_a$$

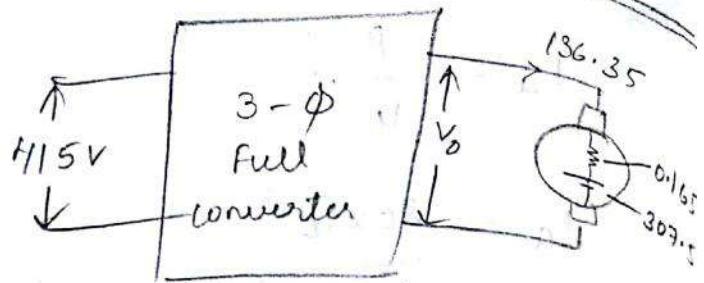

$$V_o = 136.35 \times 0.165 + 307.5$$

$$\alpha = ?$$

$$V_o = \frac{3V_{mL}}{\pi} \cos \alpha$$

$$\Rightarrow V_o = 329.99$$

Then, 
$$V_o = \frac{3V_{mL}}{\pi} \cos \alpha$$

$$\therefore \cos \alpha = \frac{V_o \times \pi}{3V_{mL}}$$



$$\cos \alpha = \frac{329.99 \times \pi}{3 \times 415 \times \sqrt{2}}$$

$$\therefore \cos \alpha = 0.588$$

$$\Rightarrow \alpha = 53.98^\circ$$


\*  $\rightarrow$  Finding turns ratio.
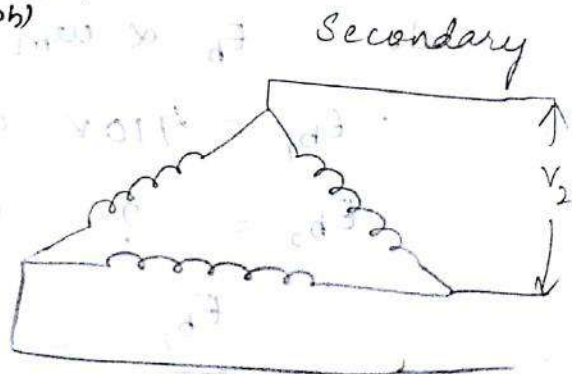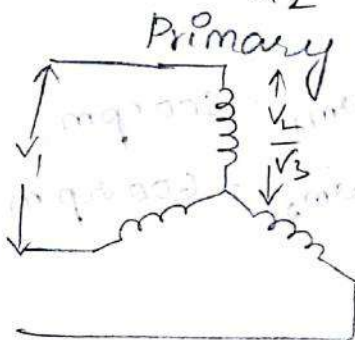
$$\frac{N_1}{N_2} = \frac{V_1(\text{ph})}{V_2(\text{ph})}$$



$$\frac{N_1}{N_2} = \frac{V_1}{\sqrt{3}V_2} \left[ V_{ph} = \frac{V_L}{\sqrt{3}} \right]$$

$$\left[ V_L = V_{ph} \right]$$

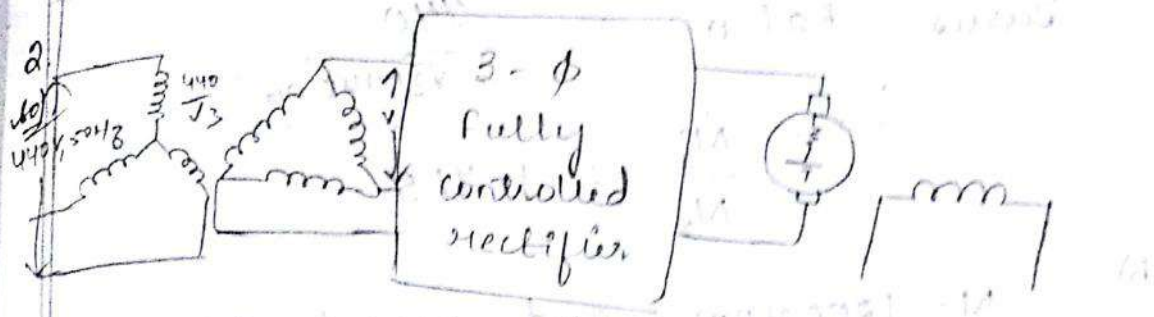


Motor terminal voltage = Rated voltage when  $\alpha = 0^\circ$ .

Motor ratings :-

200V, 1500rpm, 50A.

$R_a = 0.5 \Omega$ .

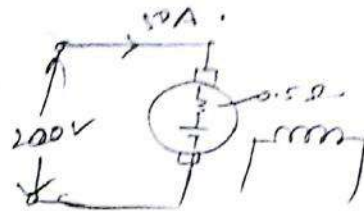

$$E_b = K_e \phi \omega_m$$

$$\Rightarrow V = I_a R_a + E_b$$

$$\Rightarrow 200 = 50 \times 0.5 + E_b$$

$$\Rightarrow E_b = 200 - 25$$

$$\therefore E_b = 175 \text{ V.}$$

a)  $\frac{N_1}{N_2} = \frac{V_1(\text{ph})}{\sqrt{3} V_2(\text{ph})}$

$$V_1 = \frac{440}{\sqrt{3}} = 254.03 \text{ V}$$

As we know that,

$$V_0 = \frac{3 V_{mL} \cos \alpha}{\pi}$$

At  $\alpha = 0^\circ$ ,  $V_0 = 200 \text{ V.}$

$$200 = \frac{3 V_{mL}}{\pi} \times 1$$

$$\Rightarrow V_{mL} = \frac{200 \times \pi}{3}$$

$$V_{mL} = 209.43 \text{ V.}$$

$$\Rightarrow V_L = \frac{V_{mL}}{\sqrt{2}} = 148.06 \text{ V.}$$

$$\text{Turns Ratio} = \frac{440}{\sqrt{3} \times 148.06}$$


$$\therefore \frac{N_1}{N_2} = 1.715$$

b)  $N_1 = 1200 \text{ rpm}$  and rated torque

$\alpha = ?$

$$E_{b1} = 175 \text{ V at } N_1 = 1500 \text{ rpm}$$
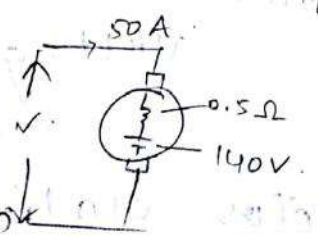
$$E_{b2} = ? \text{ at } N_2 = 1200 \text{ rpm}$$



$$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$\Rightarrow E_{b2} = E_{b1} \times \frac{N_2}{N_1} = 175 \times \frac{1200}{1500}$$

$$\Rightarrow E_{b2} = 140 \text{ V}$$

$$\Rightarrow V = E + I_a R_a$$

$$V_0 = 140 + 50 \times 0.5$$

$$V_0 = 165 \text{ V}$$

$$\Rightarrow V_0 = \frac{3 V_m \cos \alpha}{\pi}$$

$$\cos \alpha = \frac{165 \times \pi}{3 \times \sqrt{2} \times 148.06}$$

$$\cos \alpha = 0.825$$

$$\alpha = 34.41^\circ$$

c)  $N_1 = -800 \text{ rpm}$ , twice the rated torque  
 $\alpha = ?$



$$E_{b1} = 175 \text{ V at } N_1 = 1500 \text{ rpm}$$

$$E_{b3} = ? \text{ at } N_3 = -800 \text{ rpm.}$$

$$\Rightarrow \frac{E_{b1}}{E_{b3}} = \frac{N_1}{N_3}$$

$$E_{b3} = E_{b1} \times \frac{N_3}{N_1} = 175 \times \frac{-800}{1500}$$

$$\Rightarrow E_{b3} = -93.33 \text{ V.}$$

$\therefore$  twice rated torque

$$= \text{twice current} = 2(50) = 100 \text{ A.}$$

$$\Rightarrow V_0 = E + I_a R_a$$

$$V_0 = -93.33 + 100 \times 0.5$$

$$V_0 = -43.33 \text{ V.}$$


$$\Rightarrow V_0 = \frac{3V_m \cos \alpha}{\pi}$$

$$\frac{-43.33 \times \pi}{3 \times \sqrt{2} \times 148.06} = \cos \alpha$$

$$\cos \alpha = -0.216$$

$$\alpha = 102.47^\circ$$

5. Given that,

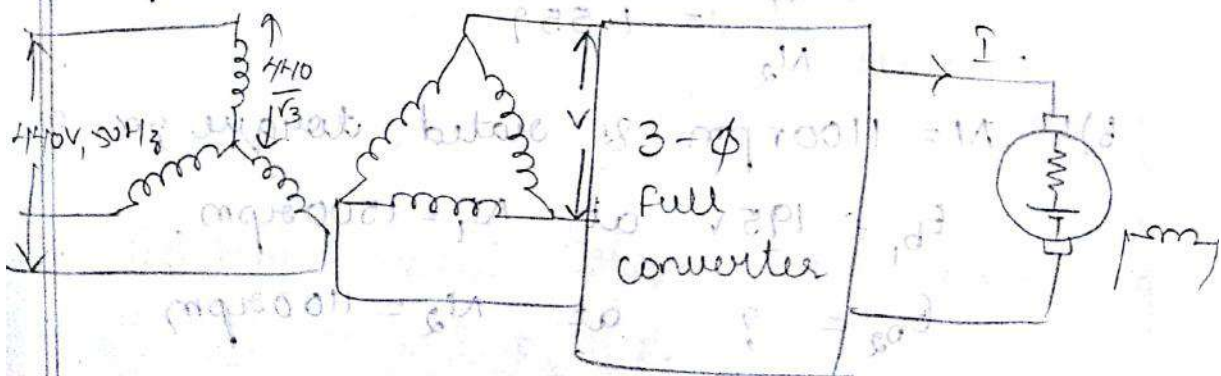

Motor terminal voltage

= Rated voltage when  $\alpha = 0^\circ$ .

Motor ratings:


220V, 1500 rpm, 50A;  $R_a = 0.5 \Omega$ .

$$\Rightarrow V = I_a R_a + E_b$$

$$220 = 50 \times 0.5 + E_b$$

$$\Rightarrow E_b = 220 - 25$$

$$\Rightarrow E_b = 195 \text{ V}$$

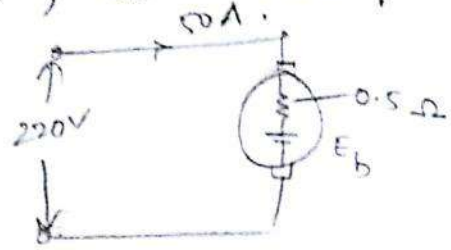

a)  $\frac{N_1}{N_2} = \frac{V_1(\text{ph})}{V_2(\text{ph})}$

$$\Rightarrow V_0 = \frac{3 V_{ml} \cos \alpha}{\pi}$$

at  $\alpha = 0^\circ$ ,  $V_0 = 220 \text{ V}$ .

$$220 = \frac{3 V_{ml}}{\pi}$$

$$\Rightarrow V_{ml} = \frac{220 \times \pi}{3}$$

$$\therefore V_{ml} = 230.37 \text{ V}$$

$$\Rightarrow V_L = \frac{V_{ml}}{\sqrt{2}} = 162.90 \text{ V}$$

$$\Rightarrow \frac{N_1}{N_2} = \frac{440}{\sqrt{3} \times 162.90}$$

$$\therefore \frac{N_1}{N_2} = 1.559$$

b)  $N = 1100 \text{ rpm}$  & stated torque;  $\alpha = ?$

$$E_{b1} = 195 \text{ V at } N_1 = 1500 \text{ rpm}$$

$$E_{b2} = ? \text{ at } N_2 = 1100 \text{ rpm}$$

Since  $E_b \propto N$

$$\Rightarrow \frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$\Rightarrow E_{b2} = E_{b1} \times \frac{N_2}{N_1} = 195 \times \frac{1100}{1500}$$

$$\therefore E_{b2} = 143 \text{ V.}$$

Rated torque = Rated current

$$= 50 \text{ A.}$$

$$\Rightarrow V_o = I_a R_a + E_b.$$

$$\therefore V_o = 0.5 \times 50 + 143.$$

$$\Rightarrow V_o = 168 \text{ V.}$$

$$\Rightarrow V_o = \frac{3V_{me} \cos \alpha}{\pi}$$

$$\cos \alpha = \frac{V_o \times \pi}{3V_{me}} = \frac{168 \times \pi}{3 \times \sqrt{2} \times 162.90}$$

$$\therefore \cos \alpha = 0.763.$$

$$\Rightarrow \alpha = 40.27^\circ$$

c)  $N = -850 \text{ rpm}$ ; 1.5 times rated torque.

$$E_{b1} = 195 \text{ V at } N_1 = 1500 \text{ rpm.}$$

$$E_{b3} = ? \text{ at } N_3 = -850 \text{ rpm.}$$

$$\frac{E_{b1}}{E_{b3}} = \frac{N_1}{N_3}$$

$$\Rightarrow E_{b3} = E_{b1} \times \frac{N_3}{N_1} = 195 \times \frac{-850}{1500}$$


$$\therefore E_{b3} = -110.5 \text{ V.}$$

$$1.5 \text{ times rated torque} = 1.5 \times 50 = 75 \text{ A.}$$

$$\therefore V_o = I_a R_a + E_b.$$

$$V_o = 0.5 \times 75 + (-110.5).$$

$$V_b = -118.75 \text{ V.}$$

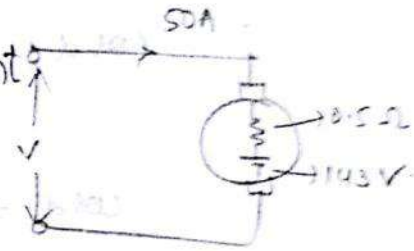




$$V_0 = -73 \text{ V}$$

$$\therefore V_0 = \frac{3V_{ml}}{\pi} \cos \alpha$$


$$\cos \alpha = \frac{V_0 \times \pi}{3V_{ml}} = \frac{-73 \times \pi}{3 \times \sqrt{2} \times 168.09}$$

$$\cos \alpha = -0.33$$

$$\Rightarrow \alpha = 109.45^\circ$$

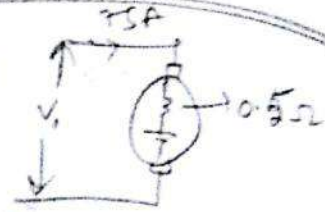

6.

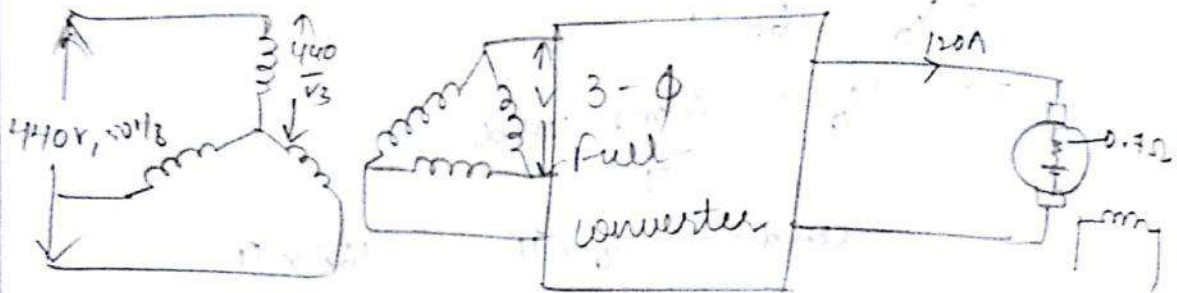

Motor ratings:

220V, 1440 rpm, 120A.

$$R_a = 0.7 \Omega$$

Motor terminal voltage = Rated voltage when  $\alpha = 0^\circ$ .

$$V = I_a R_a + E_b$$

$$220 = 120 \times 0.7 + E_b$$

$$E_b = 220 - 84$$


$$\therefore E_b = 136 \text{ V}$$

$$a) \frac{N_1}{N_2} = \frac{V_1 (\text{ph})}{V_2 (\text{ph})}$$

$$V_0 = \frac{3V_{ml}}{\pi} \cos \alpha$$

$$\text{At } \alpha = 0^\circ, V_0 = 220 \text{ V}$$

$$\frac{220 \times \pi}{3} = 3V_{ml}$$

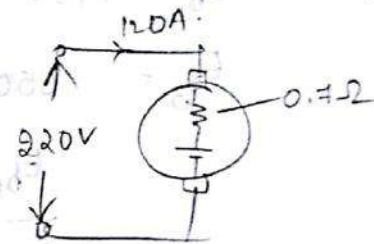

$$\Rightarrow V_{m2} = 230.37 \text{ V.}$$

$$\therefore V_L = \frac{V_{m2}}{\sqrt{2}} = 162.90 \text{ V.}$$

$$\Rightarrow \frac{N_1}{N_2} = \frac{440}{\sqrt{3} \times 162.90}$$

$$\therefore \frac{N_1}{N_2} = 1.55.$$

b)  $N = -900 \text{ rpm}$  at rated torque.

$$E_{b1} = 136 \text{ V at } N_1 = 1440 \text{ rpm.}$$

$$E_{b2} = ? \text{ at } N_2 = -900 \text{ rpm.}$$

$$\text{Then, } \frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$\therefore E_{b2} = E_{b1} \times \frac{N_2}{N_1} = 136 \times \frac{-900}{1440}$$

$$\Rightarrow E_{b2} = -85 \text{ V.}$$

Rated torque = Rated current = 120 A.

$$\Rightarrow V_0 = I_a R_a + E_b$$

$$V_0 = 120 \times 0.7 - 85$$


$$V_0 = -1 \text{ V}$$


$$\text{Then, } V_0 = \frac{3 V_{m2} \cos \alpha}{\pi}$$

$$\cos \alpha = \frac{-1 \times \pi}{3 \times \sqrt{2} \times 162.90}$$

$$\cos \alpha = -0.0045$$

$$\therefore \alpha = 90.25^\circ$$

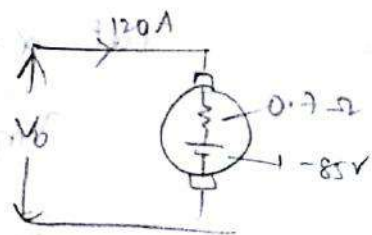

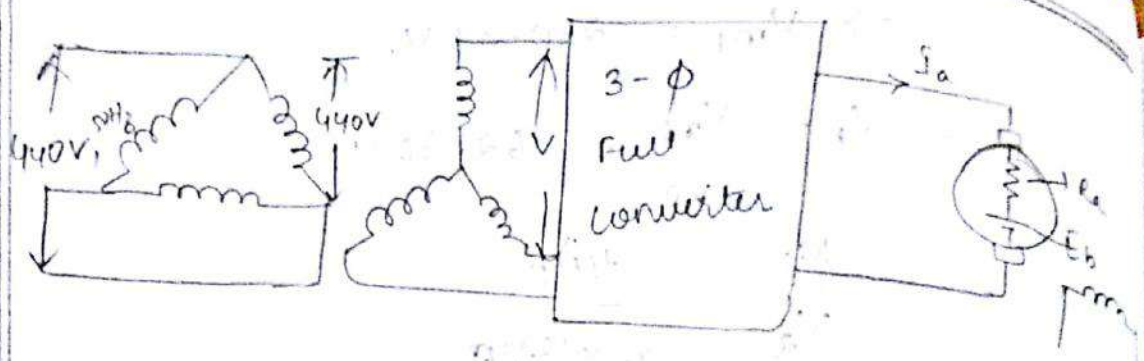

Motor terminal voltage = Rated voltage at  $\alpha = 0^\circ$ .

Motor ratings:


230V, 1500rpm, 20A;  $R_a = 0.6 \Omega$

$$V = I_a R_a + E_b$$

$$\Rightarrow E_b = 230 - 20 \times 0.6$$

$$E_b = 230 - 12$$

$$\therefore E_b = 218 \text{ V}$$

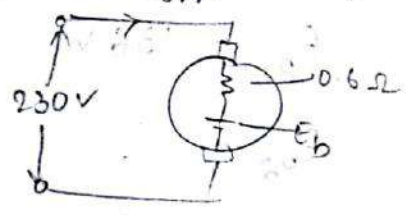

i)  $\frac{N_1}{N_2} = \frac{V_1(\text{ph})}{V_2(\text{ph})}$

$$\Rightarrow V_0 = \frac{3V_{ml} \cos \alpha}{\pi}$$

at  $\alpha = 0^\circ$ ;  $V_0 = 230 \text{ V}$ .

$$\therefore V_{ml} = \frac{230 \times \pi}{3}$$

$$V_{ml} = 240.84 \text{ V}$$

$$\Rightarrow V_l = \frac{V_{ml}}{\sqrt{2}} = 170.30 \text{ V}$$

Then,

$$\frac{N_1}{N_2} = \frac{\sqrt{3} V_l}{V_2} = \frac{440}{98.32}$$

$$\frac{N_1}{N_2} = \frac{\sqrt{3} \times 440}{170.30}$$

$$\therefore \frac{N_1}{N_2} = 4.47$$



ii)  $N = -900 \text{ rpm}$ ,  $\frac{1}{2}$  of rated torque.

$$E_{b1} = 218 \text{ V} \quad \text{at } N_1 = 1500 \text{ rpm.}$$

$$E_{b2} = ? \quad \text{at } N_2 = -900 \text{ rpm.}$$

$$\text{Then, } \frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$\Rightarrow \therefore E_{b2} = E_{b1} \times \frac{N_2}{N_1} = 218 \times \frac{-900}{1500}$$


$$\Rightarrow E_{b2} = -130.8 \text{ V}$$

Then,  $\frac{1}{2}$  Rated torque =  $\frac{1}{2} \times 20 = 10 \text{ A}$ .

$$V_0 = I_a R_a + E_b$$

$$V_0 = 0.6 \times 10 - 130.8$$

$$V_0 = -124.8 \text{ V}$$

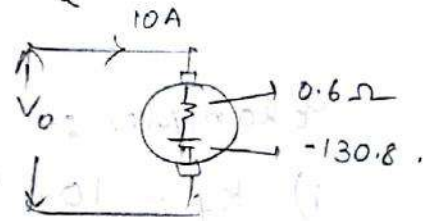

$$\text{Then, } V_0 = \frac{3 V_{mL}}{\pi} \cos \alpha$$

$$\cos \alpha = \frac{-124.8 \times \pi}{3 \times 240.84}$$

$$\cos \alpha = -0.542$$

$$\Rightarrow \alpha = 122.81^\circ$$

0/02/16

\* Understanding the constants:

$$E_b = k_e \phi \omega_m$$

$$k_e = \frac{E_b}{\phi \omega_m} = \frac{\text{V-sec}}{\text{wb-rad}}$$

$$E_b = k_g \cdot \phi \omega_m$$

$$T = k_e \phi I_a$$

$$k_e = \frac{T}{\phi I_a} = \frac{\text{N-m-sec}}{\text{wb-A}}$$

we know that,

$$\phi \propto I_f$$

$$\omega_m - \text{rad/sec}$$

$$\phi - \text{weber}$$

$$E_b - V$$

$$E_b = k_e I_f \omega_m$$

$$k_e = \frac{E_b}{I_f \omega_m} = \frac{V\text{-sec}}{A\text{-radian}}$$

→ Separately excited Motor :

$$\phi = \text{constant}$$

$$E_b = k \cdot \omega_m \quad [\because k = k_e \phi]$$

$$\therefore k = \frac{E_b}{\omega_m} = \frac{V\text{-sec}}{\text{rad}} \quad \left[ \begin{array}{l} \omega_m = \frac{6 \text{ V-sec}}{\text{rad}} \\ E_b = k_L \cdot \omega_m \end{array} \right]$$

Examples :-

i)  $k_f = 10 \frac{V\text{-sec}}{A\text{-rad}}$

Then,  $E_b = k_f I_f \omega_m$

$$E_b = k_f \phi \omega_m$$

$$k_f = \frac{E_b}{\phi \cdot \omega_m} = \frac{E_b}{I_f \cdot \omega_m}$$

$$k_f = \frac{V\text{-sec}}{\omega_b\text{-rad}} = \frac{V\text{-sec}}{A\text{-rad}}$$

ii)  $k_m = 6 \frac{V\text{-sec}}{\omega_b\text{-rad}}$

$$k_m = \frac{E_b}{\phi \omega_m} = \frac{V\text{-sec}}{\omega_b\text{-rad}}$$

$$\therefore E_b = k_m \phi \omega_m$$

iii)  $k_L = 3 \frac{V\text{-sec}}{A\text{-rpm}}$


$$E_b = k_L I_f N$$

$$k_L = \frac{V}{A \cdot \text{rpm}}$$

$$iv) \quad k_c = 9 \frac{\text{v-sec}}{\text{rad}}$$

$$E_b = k_c \cdot \omega_m$$

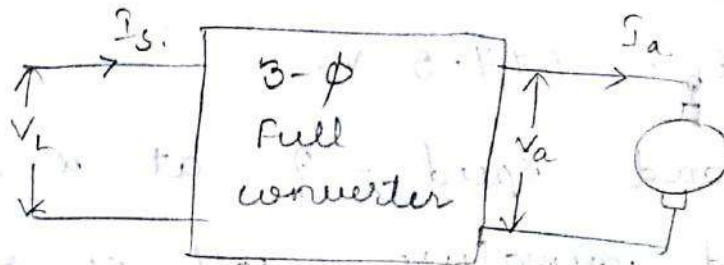\* Finding a power factor of a converter:



$$V_a I_a = 3 \sqrt{3} V_L I_s \cos \phi$$

$$\cos \phi = \frac{V_a I_a}{3 \sqrt{3} V_L I_s}$$

→ The losses and commutation angle is neglected.

$$\text{pf} = \cos \alpha$$

where  $\alpha$  = firing angle of the system.

→ Relation between  $I_a$  &  $I_s$  in 3-φ Full Bridge Converter:

$$I_s = I_a \sqrt{\frac{2}{3}}$$



10/02/16

7.

Motor ratings

150 HP, 650 V, 1750 rpm.

Given,


$$k_a \phi = 0.33 \text{ V/rpm.}$$

Then,  $E_b = k_a \phi N.$

$$k_a \phi = \frac{E_b}{N} = \frac{V}{\text{rpm}}$$

$$\Rightarrow E_b = 0.33 \times 1750.$$

$$\therefore E_b = 577.5 \text{ V.}$$

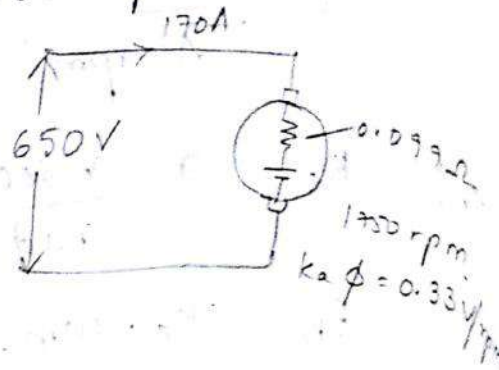


a) No-load speed = ? at  $\alpha = 30^\circ.$

At No-load, armature = 10% of rated current.

$$= 0.1 \times 170.$$

$$= 17 \text{ A.}$$

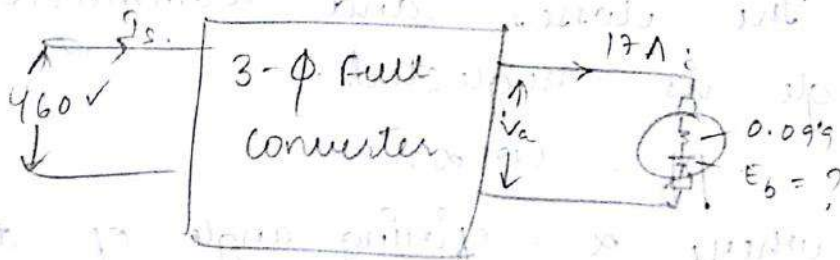

$$V_a = \frac{3V_{mL}}{\pi} \cos \alpha \quad [\alpha = 30^\circ]$$

$$V_a = \frac{3 \times 460 \times \sqrt{2}}{\pi} \cos 30^\circ$$

$$\therefore V_a = 538.00 \text{ V.}$$

Then,  $V_a = I_a R_a + E_b$ . At full load:

$$\therefore E_b = 538 - 17 \times 0.099$$

$$\therefore E_b = 536.317 \text{ V}$$

$$\Rightarrow K_a \phi N = \frac{536.317}{0.33}$$

$$N = \frac{536.317}{0.33} = 1625.20 \text{ rpm}$$

$$\therefore N_b = 1625.20 \text{ rpm}$$

b)  $\alpha = ?$  Rated speed of 1750 rpm.  
at rated motor current.

$\text{pf} = ?$

$$E_b = K_a \phi N$$

$$E_b = 0.33 \times 1750$$

$$E_b = 577.5 \text{ V}$$

Then,  $V_a = I_a R_a + E_b$

$$V_a = 170 \times 0.099 + 577.5$$

$$\therefore V_a = 594.33 \text{ V}$$

Then,  $V_a = \frac{3V_m \cos \alpha}{\pi}$

$$\cos \alpha = \frac{V_a \pi}{3V_m} = \frac{594.33 \times \pi}{3 \times 460 \times \sqrt{2}}$$

$$\cos \alpha = 0.956$$

$$\alpha = 17.05^\circ$$

Then,  $\cos \phi = \frac{V_a I_a}{3V_{ph} I_s}$

$$I_a = 170 \text{ A}$$

$$I_s = I_0 \sqrt{\frac{2}{3}}$$

$$I_s = 170 \sqrt{\frac{2}{3}}$$

$$I_s = 138.80 \text{ A}$$

$$\text{Then, } \cos \phi = \frac{V_a \cdot I_a}{3 \phi n I_s}$$

$$= \frac{594.33 \times 170}{3 \times 460 \times 138.8 \sqrt{3}}$$

$$\therefore \cos \phi = 0.913$$

c) at full load,

$$V_a = I_a R_a + E_b$$

$$\Rightarrow E_b = 538.00 - 170 \times 0.099$$

$$\therefore E_b = 521.17 \text{ V}$$

$$\text{Then, } k_a \phi N = 521.17$$

$$N = \frac{521.17}{0.33}$$

$$\therefore N_{FL} = 1579.30 \text{ rpm}$$

$$\text{Speed Regulation} = \frac{N_0 - N_{FL}}{N_0} \times 100$$

$$= \frac{1625.20 - 1579.30}{1625.20} \times 100$$


$$= 2.82\%$$



Given that, Motor ratings:  
 25 HP, 320V, 960 rpm.

$$R_a = 0.2 \Omega, R_f = 130 \Omega; k_a = 1.2 \frac{\text{V-sec}}{\text{A-rad}}$$
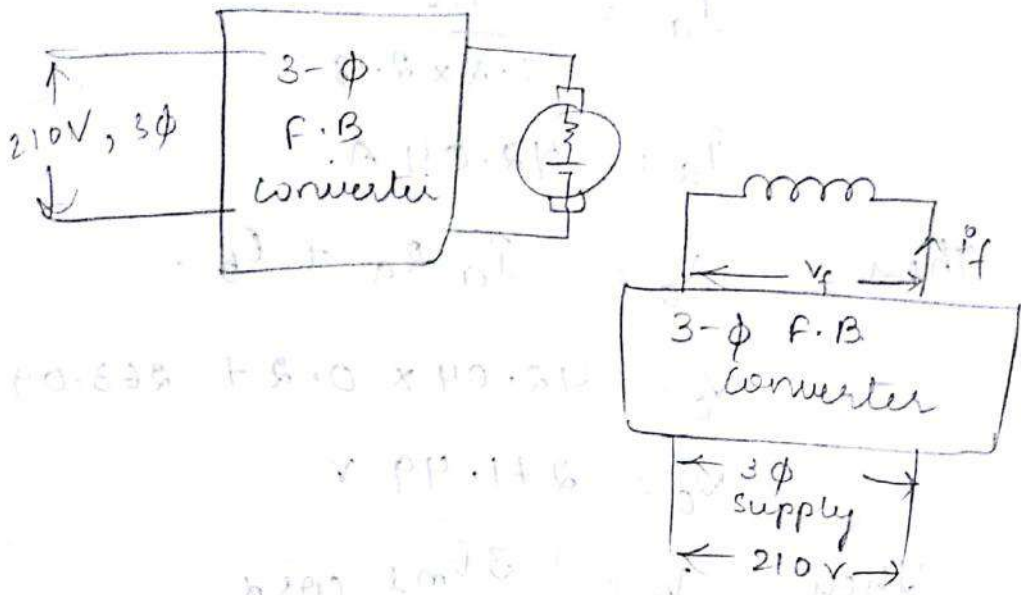
$$k_a = \frac{E_b}{I_f \cdot \omega_m} \Rightarrow E_b = k_a I_f \omega_m$$



i).

$$E_b = k_a I_f \cdot \omega_m$$

$$\omega_m = \frac{960 \times 2\pi}{60}$$

$$\omega_m = 100.528$$

$$I_f = \frac{V_f}{130} = \frac{3 \times V_{m\ell}}{\pi \times 130}$$

$$I_f = \frac{3 \times 210 \times \sqrt{2}}{\pi \times 130}$$

$$[\because V_f = \frac{3V_{m\ell}}{\pi}]$$

$$\therefore I_f = 2.18 \text{ A}$$

$$\text{Then, } E_b = 1.2 \times 2.18 \times 100.528$$

$$\therefore E_b = 263.98 \text{ V}$$

Given,  $T = 110 \text{ N-m}$ .

$$k_e \phi I_a = 110 \text{ N-m}$$

$$k_e I_f I_a = 110 \text{ N-m} \quad [\because \phi \propto I_f]$$

$$\therefore I_a = \frac{110}{k_a \cdot I_f}$$

$$\therefore I_a = \frac{110}{1.2 \times 2.18}$$

$$\therefore I_a = 42.04 \text{ A}$$

Then,  $V_0 = I_a R_a + E_b$

$$V_0 = 42.04 \times 0.2 + 263.09$$

$$V_0 = 271.49 \text{ V}$$

Then,  $V_0 = \frac{3 V_{ml} \cos \alpha}{\pi}$

$$\cos \alpha = \frac{271.49 \times \pi}{3 \times 210 \times \sqrt{2}}$$

$$\cos \alpha = 0.957$$

$$\therefore \alpha = 16.86^\circ$$

ii)

$\alpha = ?$ ,  $T = 110 \text{ N-m}$ .

$$\alpha = 0^\circ$$

Then  $T = k_a I_f I_a \Rightarrow I_a = \frac{T}{k_a I_f}$

$$\therefore I_a = 42.04 \text{ A}$$

$$V_0 = \frac{3 V_{ml}}{\pi} = \frac{3 \times 210 \times \sqrt{2}}{\pi}$$

$$V_0 = 283.60 \text{ V}$$

Then,  $V_o = I_a R_a + E_b$

$$283.60 - 42.04 \times 0.2 = E_b$$

$$\Rightarrow E_b = 275.20 \text{ V}$$

$$K_a I_f \omega_m = 275.20$$

$$\omega_m = \frac{275.20}{1.8 \times 2.18}$$

$$\omega_m = 105.19$$

$$\frac{2\pi N}{60} = 105.19$$


$$N = \frac{105.19 \times 60}{2\pi}$$

$$\Rightarrow N = 1004.52 \text{ rpm}$$

2/22/16

→ iii) To find firing angle of field converter.

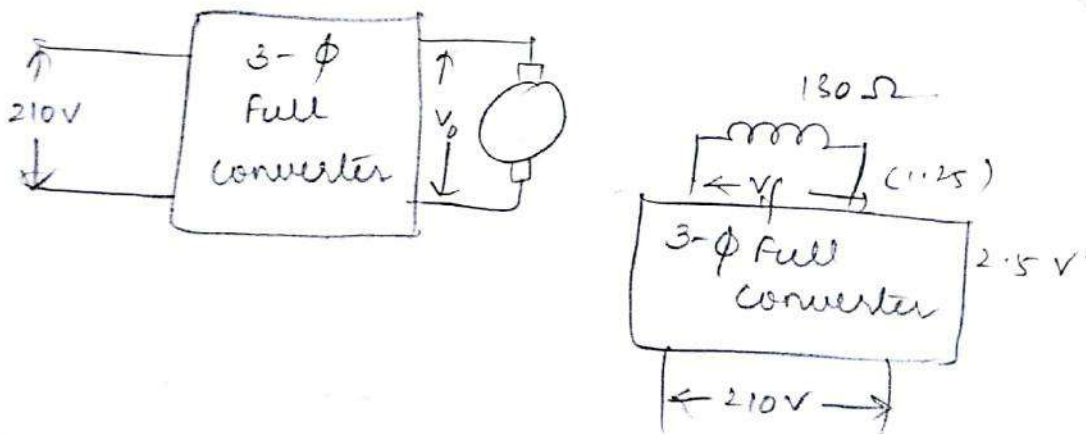For same load requirement in part (ii) at speed 1750 rpm.




→ So, here he is doing flux control by changing  $\alpha$  of field converter. Keeping remaining same

$$\Rightarrow E_b = K_a I_f \omega$$



$$275 = 1.7 I_f \left( \frac{2\pi \times 1350}{60} \right)$$

$$\therefore I_f = 1.25 \text{ A}$$

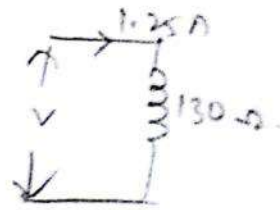

Then  $V_f = I_f \times R_f$

$$\therefore V_f = 1.25 \times 130 = 162.5 \text{ V}$$

$\therefore$  where,  $V_f = \frac{3V_m \cos \alpha}{\pi}$

$$162.5 = \frac{3 \times 210 \times \sqrt{2}}{\pi} \cos \alpha$$

$$\cos \alpha = \frac{162.5 \times \pi}{3 \times 210 \times \sqrt{2}}$$

$$\cos \alpha = 0.572$$


$$\Rightarrow \alpha = 55.11^\circ$$

21/02/16

Problems :

\* The chopper is operated for both motoring & braking operation.

→ Motoring Mode:

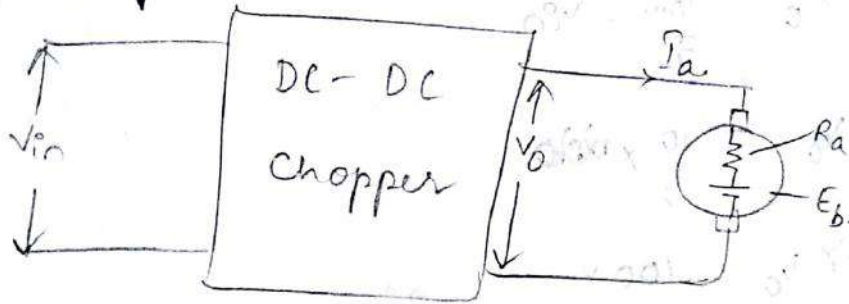


Then,  $V_o = \delta \cdot V_{in}$

$\Rightarrow V_o = I_a R_a + E_b$

Then,  $\delta \cdot V_{in} = I_a R_a + E_b$

→ Braking Mode:

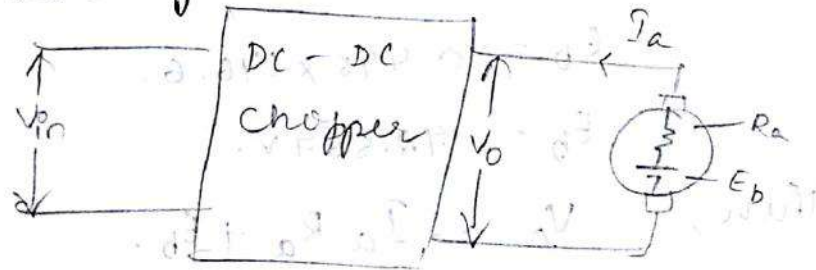

$V_o = \delta \cdot V_{in}$

$\Rightarrow E_b = I_a R_a + V_o$

$\therefore E_b = I_a R_a + \delta \cdot V_{in}$

$V_s = 220V$

$T_{ON} = 10msec$


$R_a = 2\Omega$

$T_{OFF} = 12msec$

$I_o(avg) = ?$

$\omega_m = 146.6 \text{ rad/sec}$

$K_a = 0.495 \text{ V/rad/sec}$

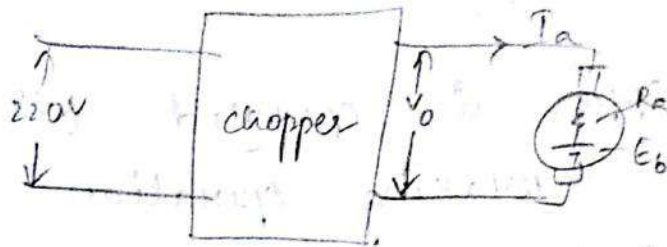

$$V_o = \frac{T_{ON}}{T} \cdot V_{in}$$

$$V_o = \frac{10}{22} \times 220$$

$$\Rightarrow V_o = 100 \text{ V}$$

Then,  $K_a = 0.495 \frac{\text{V-sec}}{\text{rad}}$

$$K_a = \frac{E_b}{\omega_m}$$

$$\therefore E_b = K_a \omega_m$$

$$E_b = 0.495 \times 146.6$$

$$E_b = 72.567 \text{ V}$$

Then,  $V_o = I_a R_a + E_b$

$$\frac{V_o - E_b}{R_a} = I_a$$


$$\therefore I_a = \frac{100 - 72.567}{2}$$

$$\Rightarrow I_a = 13.717 \text{ A}$$

230V, 960rpm, 200A,  $R_a = 0.02 \Omega$

i) FOR MOTORING MODE :-




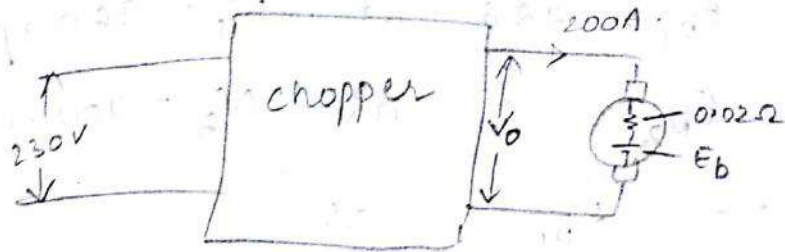

$$V_o = I_a R_a + E_b.$$

$$230 = 200 \times 0.02 + E_b.$$

$$\therefore E_b = 226 \text{ V.}$$

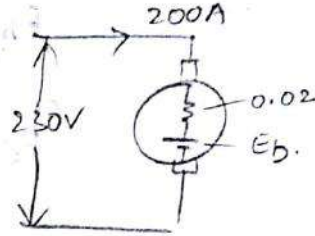

i) Then,  $E_{b1} = 226 \text{ V}$  at 960 rpm.

$E_{b2} = ?$  at 450 rpm.

$$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$\Rightarrow E_{b2} = 226 \times \frac{450}{960}$$

$$\Rightarrow E_{b2} = 105.93 \text{ V.}$$

Then,  $V_o = I_a R_a + E_b.$

$$V_o = 200 \times 0.02 + 105.93.$$

$$\Rightarrow V_o = 109.93 \text{ V.}$$

$$\therefore V_{in} = 109.93.$$

$$\Rightarrow \delta = \frac{109.93}{230}$$

$$\therefore \delta = 0.47.$$

ii) FOR BRAKING MODE:


Rated torque and 450 rpm.

$$E_{b1} = 226 \text{ at } N_1 = 960 \text{ rpm.}$$

$$E_{b3} = ? \text{ at } N_3 = 400 \text{ rpm.}$$

$$\Rightarrow \frac{E_{b1}}{E_{b3}} = \frac{N_1}{N_3}$$

$$E_{b3} = \frac{226 \times 400}{960}$$

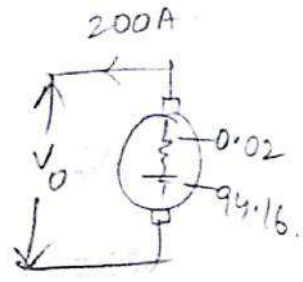

$$\therefore E_{b3} = 94.16 \text{ V}$$

Then,  $V_0 + I_a R_a = E_b$

$$V_0 = E_b - I_a R_a$$

$$V_0 = 94.16 - 200 \times 0.02$$

$$V_0 = 90.16 \text{ V}$$

$$\Rightarrow \delta \cdot V_{in} = 90.16$$

$$\delta = \frac{90.16}{230}$$

$$\delta = 0.392$$

iii)  $\delta_{max} = 0.95$

Max. permissible motor current is twice the rated.

$$V_0 = \delta \cdot V_{in}$$

$$V_0 = 0.95 \times 230$$

$$\therefore V_0 = 218.5$$

Then,  $E_b = V_0 + I_a R_a$

$$E_b = 218.5 + 400 \times 0.02$$

$$E_b = 226.5$$

Then,  $E_{b1} = 226 \text{ V}$  at  $N_1 = 960 \text{ rpm}$ .

$E_{b2} = 226.5 \text{ V}$  at  $N_2 = ?$

$$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$\Rightarrow N_2 = \frac{E_{b2}}{E_{b1}} \times N_1$$


$$\Rightarrow N_2 = 962.12 \text{ rpm.}$$

5.11) Given that,

220 V, 24 A, 1000 rpm.,  $R_a = 2 \Omega$ .

$f = 500 \text{ Hz}$  &  $V_s = 230 \text{ V}$ .

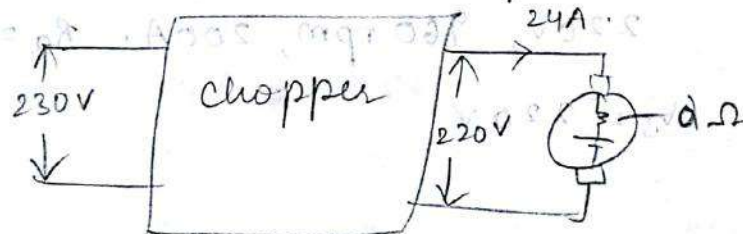
$\delta = ?$  for 1.2 times rated torque  
& 500 rpm.



$$V_o = I_a R_a + E_b$$

$$\therefore 220 = 24 \times 2 + E_b$$
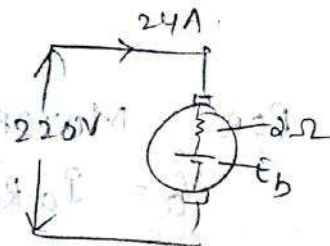
$$\therefore \boxed{E_b = 172 \text{ V.}}$$



Then,  $E_{b1} = 172 \text{ V}$  at  $N_1 = 1000 \text{ rpm}$ .

$E_{b2} = ?$  at  $N_2 = 500 \text{ rpm}$ .

$$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$\Rightarrow E_{b2} = \frac{E_{b1}}{N_1} \times N_2 = \frac{172 \times 500}{1000}$$



$$\Rightarrow E_{b2} = 86V.$$

1.2 times rated torque

$$= 1.2 \text{ rated current.}$$

$$= 1.2 \times 24.$$

$$= 28.8 A.$$


then,  $V_0 = I_a R_a + E_b.$

$$V_0 = 28.8 \times 2 + 86.$$

$$\therefore V_0 = 143.6 V.$$

$$\delta \cdot V_{in} = 143.6 V. \Rightarrow \delta = \frac{143.6}{230}$$


$$\Rightarrow \delta = 0.624$$

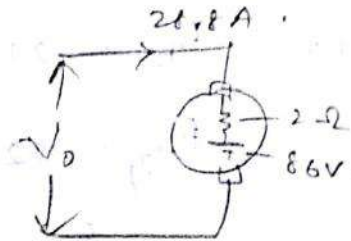

8. Given that,

220V, 960 rpm, 200A.  $R_a = 0.02 \Omega.$

$$V_s = 220 V.$$

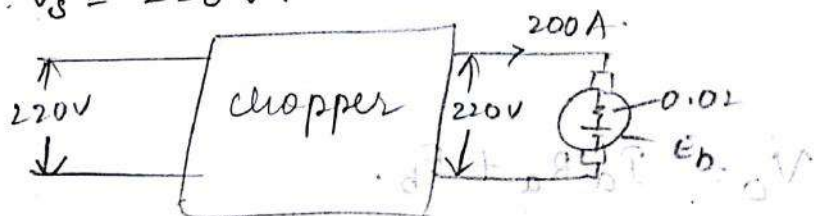

i) FOR MOTORING MODE:

$$V_0 = I_a R_a + E_b.$$

$$220 = 200 \times 0.02 + E_b.$$

$$\therefore E_b = 216 V.$$

then,  $E_{b1} = 216 V$  at  $N_1 = 960 \text{ rpm.}$

$E_{b2} = ?$  at  $N_2 = 400 \text{ rpm.}$

$$\Rightarrow \frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

